



GATE 2023

ELECTRONICS
ENGINEERING

Questions
& Solutions



Corporate Office: 44-A/1, Kalu Sarai, New Delhi-110016
MADE EASY Centres : Delhi , Hyderabad , Jaipur, Bhopal,
Lucknow, Bhubaneswar, Pune, Kolkata



9021300500



www.madeeasy.in

Exam held
on 05th Feb, 2023
Afternoon
Session

SECTION - A

GENERAL APTITUDE

Q.1 "I cannot support this proposal. My _____ will not permit it."

- (a) conscious
- (b) consensus
- (c) conscience
- (d) consent

[1 Mark : MCQ]

Ans. (c)

End of Solution

Q.2 Courts : _____ :: Parliament : Legislature

- (a) Judiciary
- (b) Executive
- (c) Governmental
- (d) Legal

[1 Mark : MCQ]

Ans. (a)

End of Solution

Q.3 What is the smallest number with distinct digits whose digits add up to 45?

- (a) 123555789
- (b) 123457869
- (c) 123456789
- (d) 99999

[1 Mark : MCQ]

Ans. (c)

The digits should be distinct and smallest number is 123456789.

End of Solution

Q.4 In a class of 100 students,

- (i) there are 30 students who neither like romantic movies nor comedy movies,
- (ii) the number of students who like romantic movies is twice the number of students who like comedy movies, and
- (iii) the number of students who like both romantic movies and comedy movies is 20.

How many students in the class like romantic movies?

- (a) 40
- (b) 20
- (c) 60
- (d) 30

[1 Mark : MCQ]

Ans. (c)

Let students who like Romantic Movies = R .

Students who like Comedy Movies = C .

Given $R = 2C$

Also, 30 students do not like Romantic and Comedy Movies both.

$$\therefore 100 - 30 = 70 = n(R \cap C)$$

$$\text{and } n(C \cap R) = 20$$

$$n(R \cap C) = n(R) + n(C) - n(C \cap R)$$

$$70 = 2C + C - 20$$



NST-2 NATIONAL SCHOLARSHIP TEST 2024

For **ESE, GATE & PSUs 2024**
Offline & Online Long-Term Courses

Register at : www.madeeasy.in

Last Date to Register (Online) : **21st Feb, 2023**

Test Date (Online) : **27th Feb, 2023**

Time Duration
45 Minutes

Total Questions
50 Questions

Total Marks
100 Marks

Negative Marking
0.66 Marks

Streams
CE, ME, EE, EC, CS, CH

9021300500

nst@madeeasy.in

nst.madeeasy.in

Scan to
Register



Scholarship applicable on batches commencing between
1st March, 2023 to 31st May, 2023


Delhi Centre : 44 - A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi - 110016 | **Ph :** 9021300500

MADE EASY Centres : Delhi | Hyderabad | Jaipur | Bhopal | Lucknow | Bhubaneswar | Pune | Kolkata | www.madeeasy.in

$$3C = 90 \\ C = 30 \\ R = 2C = 60$$

End of Solution

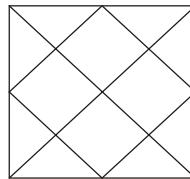Q.5 How many rectangles are present in the given figure?



- (a) 8 (b) 9
(c) 10 (d) 12

[1 Mark : MCQ]

Ans. (c)

Number of rectangles = 10 as square is also called as rectangle.

End of Solution

Q.6 Forestland is a planet inhabited by different kinds of creatures. Among other creatures, it is populated by animals all of whom are ferocious. There are also creatures that have claws, and some that do not. All creatures that have claws are ferocious.

Based only on the information provided above, which one of the following options can be logically inferred with certainty?


- (a) All creatures with claws are animals.
(b) Some creatures with claws are non-ferocious.
(c) Some non-ferocious creatures have claws.
(d) Some ferocious creatures are creatures with claws.

[2 Marks : MCQ]

Ans. (d)

End of Solution

Q.7 Which one of the following options represents the given graph?

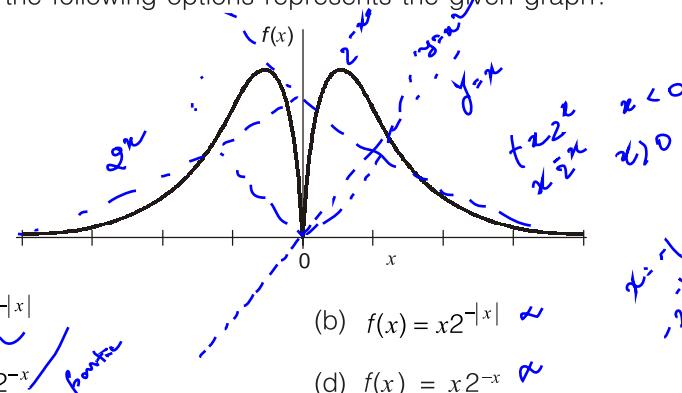**[2 Marks : MCQ]**

Ans. (a)

Since, the given function is an even function.

Option (d) is only represents the even function.

End of Solution

Q.8 Which one of the following options can be inferred from the given passage alone?

When I was a kid, I was partial to stories about other worlds and interplanetary travel. I used to imagine that I could just gaze off into space and be whisked to another planet.

[Excerpt from The Truth about Stories by T. King]

- (a) It is a child's description of what he or she likes.
- (b) It is an adult's memory of what he or she liked as a child.
- (c) The child in the passage read stories about interplanetary travel only in parts.
- (d) It teaches us that stories are good for children.

[2 Marks : MCQ]

Ans. (b)

End of Solution

Q.9 Out of 1000 individuals in a town, 100 unidentified individuals are covid positive. Due to lack of adequate covid-testing kits, the health authorities of the town devised a strategy to identify these covid-positive individuals. The strategy is to:

- (i) Collect saliva samples from all 1000 individuals and randomly group them into sets of 5.
- (ii) Mix the samples within each set and test the mixed sample for covid.
- (iii) If the test done in (ii) gives a negative result, then declare all the 5 individuals to be covid negative.
- (iv) If the test done in (ii) gives a positive result, then all the 5 individuals are separately tested for covid.

Given this strategy, no more than _____ testing kits will be required to identify all the 100 covid positive individuals irrespective of how they are grouped.

- | | |
|---------|----------|
| (a) 700 | (b) 600 |
| (c) 800 | (d) 1000 |

[2 Marks : MCQ]

Ans. (a)

*one covid individual
in each 100 group
100 + 100fif + 100 remaining*

End of Solution


Q.10 100 cm × 32 cm rectangular sheet is folded 5 times. Each time the sheet is folded, the long edge aligns with its opposite side. Eventually, the folded sheet is a rectangle of dimensions 100 cm × 1 cm.

The total number of creases visible when the sheet is unfolded is _____.

- | | |
|--------|--------|
| (a) 32 | (b) 5 |
| (c) 31 | (d) 63 |

[2 Marks : MCQ]

Ans. (c)

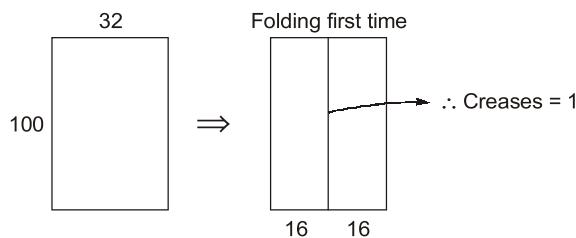

$$\therefore \text{After folding 5 times} = 1 + 2^1 + 2^2 + 2^3 + 2^4 \\ = 1 + 2 + 4 + 8 + 16 = 31$$

End of Solution

SECTION - B
TECHNICAL

- Q.11** Let $v_1 = \begin{bmatrix} 1 \\ 2 \\ 0 \end{bmatrix}$ and $v_2 = \begin{bmatrix} 2 \\ 1 \\ 3 \end{bmatrix}$ be two vectors. The value of the coefficient α in the expression

$v_1 = \alpha v_2 + e$, which minimizes the length of the error vector e , is

- | | |
|-------------------|--------------------|
| (a) $\frac{7}{2}$ | (b) $-\frac{2}{7}$ |
| (c) $\frac{2}{7}$ | (d) $-\frac{7}{2}$ |

[1 Mark : MCQ]

Ans. (c)

$$e = V_1 - \alpha V_2$$

$$e = (i + 2k + 0k) - \alpha(2i + j + 3k)$$

$$\hat{e} = (1-2\alpha)\hat{i} + (2-\alpha)\hat{j} + (0-3\alpha)\hat{k}$$

$$|\hat{e}| = \sqrt{(1-2\alpha)^2 + (2-\alpha)^2 + (-3\alpha)^2}$$

$$|\hat{e}|^2 = 5 + 14\alpha^2 - 8\alpha \text{ to be minimum at } \frac{\partial e^2}{\partial \alpha} = 28\alpha - 8 = 0$$

$$\therefore \alpha = \frac{2}{7} \text{ stationary point}$$

End of Solution

- Q.12** The rate of increase, of a scalar field $f(x, y, z) = xyz$ in the direction $v = (2, 1, 2)$ at a point $(0, 2, 1)$ is

- | | |
|-------------------|-------------------|
| (a) $\frac{2}{3}$ | (b) $\frac{4}{3}$ |
| (c) 2 | (d) 4 |

[1 Mark : MCQ]

Ans. (b)

$$f(x, y, z) = xyz$$

$$\nabla f = \hat{i}f_x + \hat{j}f_y + \hat{k}f_z$$

$$= \hat{i}(yz) + \hat{j}(xz) + \hat{k}(xy)$$

$$\nabla f|_{(0,2,1)} = \hat{i}(2) + 0\hat{j} + 0\hat{k}$$

Directional derivative,

$$D.D = \nabla f \cdot \frac{\bar{a}}{|\bar{a}|}$$

$$= (2\hat{i} + 0\hat{j} + 0\hat{k}) \cdot \frac{(2\hat{i} + \hat{j} + 2\hat{k})}{\sqrt{2^2 + 1^2 + 2^2}} = \frac{4}{\sqrt{9}} = \frac{4}{3}$$

End of Solution



Announcing

FOUNDATION COURSES for ESE 2024 • GATE 2024

The Foundation Batches are taught comprehensively which cover the requirements of all technical-syllabus based examinations.

- ✓ Classes by experienced & renowned faculties.
- ✓ Exam oriented learning ecosystem.
- ✓ Systematic subject sequence & timely completion of syllabus.
- ✓ Result oriented teaching with comprehensive coverage.
- ✓ Comprehensive & updated study material.
- ✓ Concept of problems solving through workbooks.
- ✓ Regular performance assessment through class tests.
- ✓ Similar teaching pedagogy in online and offline classes.

OFFLINE BATCHES AT DELHI

Commencing from

- **14th Mar, 2023 • 11th April, 2023**
- **4th May, 2023 • 25th May, 2023**

LIVE-ONLINE BATCHES

Commencing from

- **15th Feb, 2023 • 14th Mar, 2023**
- **15th Apr, 2023 • 15th May, 2023**

Admissions open

Delhi Centre : 44 - A/1, Kalu Sarai, Near Hauz Khas Metro Station, New Delhi - 110016 | **Ph :** 9021300500

MADE EASY Centres : **Delhi** | **Hyderabad** | **Jaipur** | **Bhopal** | **Lucknow** | **Bhubaneswar** | **Pune** | **Kolkata** | www.madeeasy.in

Q.13 Let $w^4 = 16j$. Which of the following cannot be a value of w ?

(a) $2e^{\frac{j2\pi}{8}}$

(c) $2e^{\frac{j5\pi}{8}}$

(b) $2e^{\frac{j\pi}{8}}$

(d) $2e^{\frac{j9\pi}{8}}$

[1 Mark : MCQ]
Ans. (a)

$$\begin{aligned} w &= (2)j^{1/4} \\ w &= 2(0 + j)^{1/4} \\ w &= 2 \left[e^{j(2n+1)\pi/2} \right]^{1/4} \\ &= 2 \left[e^{j(2n+1)\pi/8} \right] \end{aligned}$$

 For $n = 0$,

$w = e^{j\pi/8}$

 For $n = 2$,

$w = 2e^{5\pi j/8}$

 For $n = 4$,

$w = 2e^{9\pi j/8}$

End of Solution

Q.14 The value of the contour integral, $\oint_C \frac{z+2}{z^2+2z+2} dz$, where the contour C is

$$\left\{ z : \left| z + 1 - \frac{3}{2}j \right| = 1 \right\}$$

- (a)
- $-\pi(1 + j)$
-
- (c)
- $\pi(1 - j)$

- (b)
- $\pi(1 + j)$
-
- (d)
- $-\pi(1 - j)$

[1 Mark : MCQ]
Ans. (b)

$$I = \oint_C \frac{z+2}{z^2+2z+2} dz; c = \left| z + 1 - \frac{3}{2}i \right| = 1$$

 Poles are given $(z + 1)^2 + 1 = 0$

$z + 1 = \pm\sqrt{-1}$

$z = -1 + j, -1 - j$

 where $-1 - i$ lies outside ' c '

$z = (-1, 1)$ lies inside ' c '.

by CRT

$$\begin{aligned} \oint_C f(z) dz &= 2\pi i \operatorname{Res}(f(z), z = -1 + j) \\ &= 2\pi i \left(\frac{z+2}{2(z+1)} \right)_{z=-1+j} \end{aligned}$$

$$= 2\pi i \left(\frac{-1+j+2}{2(-1+j+1)} \right)$$

$$= \pi(1+j)$$

End of Solution

- Q.15** Let the sets of eigenvalues and eigenvectors of a matrix B be $\{\lambda_k \mid 1 \leq k \leq n\}$ and $\{v_k \mid 1 \leq k \leq n\}$, respectively. For any invertible matrix P , the sets of eigenvalues and eigenvectors of the matrix A , where $B = P^{-1}AB$, respectively, are

- (a) $\{\lambda_k \det(A) \mid 1 \leq k \leq n\}$ and $\{Pv_k \mid 1 \leq k \leq n\}$
- (b) $\{\lambda_k \mid 1 \leq k \leq n\}$ and $\{v_k \mid 1 \leq k \leq n\}$
- (c) $\{\lambda_k \mid 1 \leq k \leq n\}$ and $\{Pv_k \mid 1 \leq k \leq n\}$
- (d) $\{\lambda_k \mid 1 \leq k \leq n\}$ and $\{P^{-1}v_k \mid 1 \leq k \leq n\}$

[1 Mark : MCQ]
Ans. (c)

$$B = P^{-1}AP$$

$$\Rightarrow A = PBP^{-1}$$

$\Rightarrow A, B$ are called matrices similar.

\Rightarrow Both A, B have same set of eigen values

But eigen vectors of A, B are different.

Let $BX = \lambda X$

$$\Rightarrow (P^{-1}AP)X = \lambda X$$

$$\Rightarrow A(PX) = \lambda(PX)$$

\therefore Eigen vectors of A are PX .

End of Solution

- Q.16** In a semiconductor, if the Fermi energy level lies in the conduction band, then the semiconductor is known as Extrinsic type.

- (a) degenerate n -type.
- (b) degenerate p -type.
- (c) non-degenerate n -type.
- (d) non-degenerate p -type.

[1 Mark : MCQ]
Ans. (a)

As the Fermi lies inside the conduction band hence it is degenerate n -type semiconductor.

End of Solution

- Q.17** For an intrinsic semiconductor at temperature $T = 0 K$, which of the following statement is true?

- (a) All energy states in the valence band are filled with electrons and all energy states in the conduction band are empty of electrons.
- (b) All energy states in the valence band are empty of electrons and all energy states in the conduction band are filled with electrons.

- (c) All energy states in the valence and conduction band are filled with holes.
 (d) All energy states in the valence and conduction band are filled with electrons.

[1 Mark : MCQ]

Ans. (a)Intrinsic semiconductor at $T = 0$ K behaves as an insulator.

Hence, valence band is completely filled with electron and conduction band is completely empty.

End of Solution

- Q.18** A series RLC circuit has a quality factor Q of 1000 at a center frequency of 10^6 rad/s. The possible values of R , L and C are
 (a) $R = 1 \Omega$, $L = 1 \mu\text{H}$ and $C = 1 \mu\text{F}$
 (b) $R = 0.1 \Omega$, $L = 1 \mu\text{H}$ and $C = 1 \mu\text{F}$
 (c) $R = 0.01 \Omega$, $L = 1 \mu\text{H}$ and $C = 1 \mu\text{F}$
 (d) $\underline{R = 0.001 \Omega}$, $L = 1 \mu\text{H}$ and $C = 1 \mu\text{F}$

[1 Mark : MCQ]


Ans. (d)Given: $Q = 1000$ and $\omega_o = 10^6$ rad/secWe know, for series RLC circuit,


$$Q = \frac{\omega_o L}{R}$$

Also,

$$\omega_o = \sqrt{\frac{1}{LC}}$$

$$Q = \frac{1}{\sqrt{LC}} \times \frac{1}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

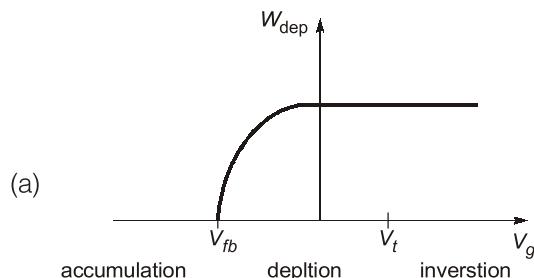So, $L = 1 \mu\text{H}$, $C = 1 \mu\text{F}$ and $R = 0.001$ **End of Solution****Q.19**For a MOS capacitor, V_{fb} and V_t are the flat-band voltage and the threshold voltage, respectively. The variation of the depletion width (W_{dep}) for varying gate voltage (V_g) is best represented by

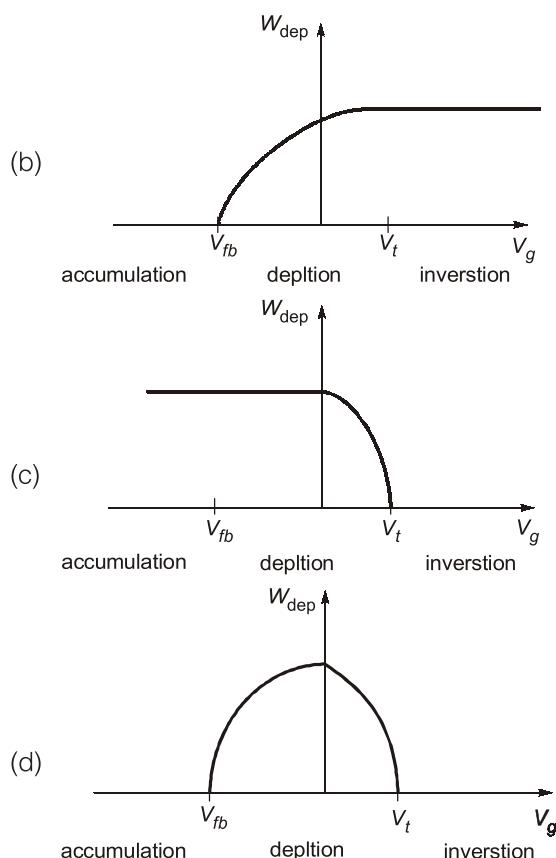
[1 Mark : MCQ]
Ans. (b)

\because We know $V_G < V_{FB}$ then accumulation mode.

\therefore In accumulation mode $W_d = 0$ because there is no depletion charge.

Now, $V_{FB} < V_G < V_t \Rightarrow$ then depletion and inversion mode.

\therefore Depletion width is available.

$\therefore V_G > V_t \Rightarrow$ Strong inversion.

\therefore Depletion width $W_d \Rightarrow$ Constant.

$$\text{And } W_d = \sqrt{\frac{2\epsilon |\phi_s|}{qN_s}} \text{ and } |\phi_s| \propto V_G$$

But after strong inversion, W_d remains constant.

\therefore Correction option is (b).

End of Solution

Q.20 Consider a narrow band signal, propagating in a lossless dielectric medium ($\epsilon_r = 4$, $\mu_r = 1$), with phase velocity v_p and group velocity v_g . Which of the following statement is true?
 (c is the velocity of light in vacuum.)

- | | |
|---------------------------|---------------------------|
| (a) $v_p > c$, $v_g > c$ | (b) $v_p < c$, $v_g > c$ |
| (c) $v_p > c$, $v_g < c$ | (d) $v_p < c$, $v_g < c$ |

[1 Mark : MCQ]


Ans. (d)

- Phase velocity, $V_p = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{\mu\epsilon}} = \frac{1}{\sqrt{\mu_0\epsilon_0}}, \frac{1}{\sqrt{\mu_r\epsilon_r}} = \frac{C}{\sqrt{\mu_r\epsilon_r}}$
 $\therefore V_p < C$
- Group velocity, $V_g = \frac{d\omega}{d\beta} = \frac{V_p}{1 - \frac{\omega}{V_p} \frac{dV_p}{d\omega}}$

Here, $V_p \neq f(\omega)$
 $\therefore V_g = V_p < C$
Hence, $V_p < C$
 $V_g < C$

End of Solution

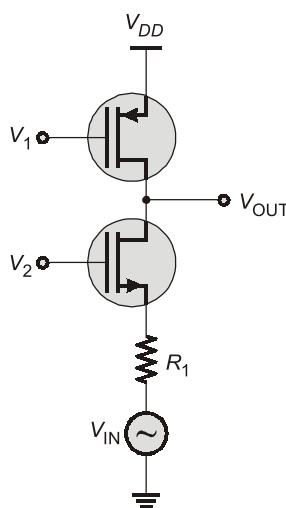Q.21 In the circuit shown below, V_1 and V_2 are bias voltages. Based on input and output impedances, the circuit behaves as a



- (a) voltage controlled voltage source. (b) voltage controlled current source.
(c) current controlled voltage source. (d) current controlled current source.

[1 Mark : MCQ]



Conventional Questions Practice Programme for ESE & State Services Exams

Commencing from
1st March, 2023

Teaching Hours :
300 to 350 hours

Course Duration :
100 days


**OFFLINE
& ONLINE
COURSE**
Streams :
CE, ME, EE, EC

Key Features

- ✓ In-depth discussion on conventional questions.
- ✓ Beneficial to develop numerical question-solving techniques.
- ✓ Helps to improve answer writing & presentation skills.
- ✓ Discussion on probable questions.
- ✓ Updated Mains workbook with wide range of practice questions.
- ✓ ESE Mains test series will be conducted on every Sunday in synchronization with the subjects.

Note : Offline classes will be conducted at Delhi Centre.

Ans. (d)

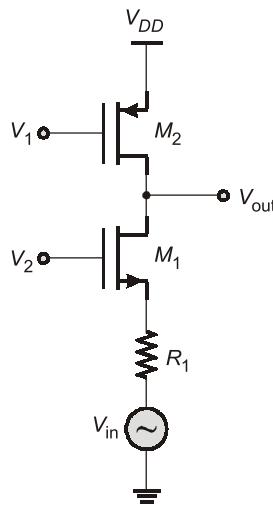

Here from circuit,

M_1 is common-gate amplifier and M_2 behaves as an active load.

By using properties of common gate (CG) amplifier,

Input impedance (R_i) is low

Output impedance (R_o) is high

So, it is a current amplifier

Current amplifier is a current controlled current source.

End of Solution

Q.22 A cascade of common-source amplifiers in a unity gain feedback configuration oscillates when

- the closed loop gain is less than 1 and the phase shift is less than 180° .
- the closed loop gain is greater than 1 and the phase shift is less than 180° .
- the closed loop gain is less than 1 and the phase shift is greater than 180° .
- the closed loop gain is greater than 1 and the phase shift is greater than 180° .

[1 Mark : MCQ]

Ans. (*)

For oscillation,


- Loop gain magnitude ≥ 1 .
- Phase of loop gain = 360°

So, correct answer is option (d).

* In options, closes loop gain is mentioned technically it should be loop gain.

End of Solution

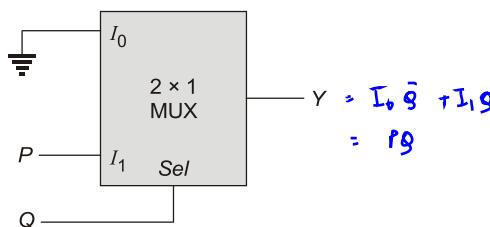- Q.23** In the circuit shown below, P and Q are the inputs. The logical function realized by the circuit shown below is



- (a) $Y = PQ$ (b) $Y = P + Q$
 (c) $Y = \overline{PQ}$ (d) $Y = \overline{P+Q}$


[1 Mark : MCQ]

Ans. (a)

$$\begin{aligned} \text{Output} &= \bar{Q} \cdot I_0 + Q \cdot I_1 \\ &= \bar{Q} \cdot 0 + Q \cdot P \\ &= PQ \end{aligned}$$

End of Solution

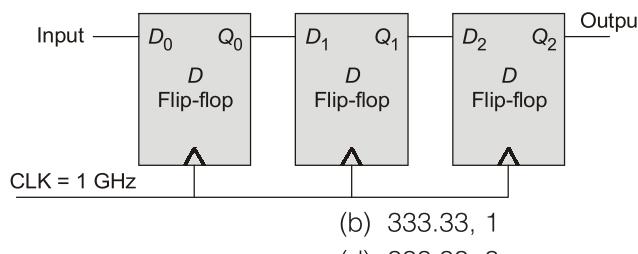- Q.24** The synchronous sequential circuit shown below works at a clock frequency of 1 GHz. The throughput, in M bits/s, and the latency, in ns, respectively, are



- (a) 1000, 3 (b) 333.33, 1
 (c) 2000, 3 (d) 333.33, 3

[1 Mark : MCQ]

Ans. (a)

The given circuit is a type of SISO.

$$\begin{aligned} \therefore \text{Latency} &= n \times T_{\text{clk}} \quad \dots \quad n = \text{number of flip flops} \\ &= 3 \times 1 \quad \dots \quad T_{\text{clk}} = \frac{1}{f_{\text{clk}}} = 1 \text{ ns} \\ &\checkmark = 3 \text{ ns} \end{aligned}$$

Now, Throughput = Number of bits/sec

$$\therefore 1 \text{ bit} = 1 \text{ nsec}$$

$$\therefore \text{Throughput} = 10^9 \text{ bits/sec} \\ = 1000 \text{ Mbps}$$

End of Solution

Q.25 The open loop transfer function of a unity negative feedback system is

$G(s) = \frac{k}{s(1+sT_1)(1+sT_2)}$, where k , T_1 and T_2 are positive constants. The phase crossover frequency, in rad/s, is

(a) $\frac{1}{\sqrt{T_1 T_2}}$

(b) $\frac{1}{T_1 T_2}$

(c) $\frac{1}{T_1 \sqrt{T_2}}$

(d) $\frac{1}{T_2 \sqrt{T_1}}$

[1 Mark : MCQ]

Ans. (a)

We know phase crossover frequency is that frequency at which phase of the open loop transfer function is -180° .

$$\therefore G(s) = \frac{K}{s(1+sT_1)(1+sT_2)}$$

$$G(j\omega) = \frac{K}{(j\omega)(1+j\omega T_1)(1+j\omega T_2)}$$

$$\text{Phase of } G(j\omega) = \phi = -90 - \tan^{-1}(\omega T_1) - \tan^{-1}(\omega T_2)$$

$$\therefore \text{At } \omega = \omega_{pc}, \phi = -180$$

$$\therefore -180 = -90 - \tan^{-1}(\omega_{pc} T_1) - \tan^{-1}(\omega_{pc} T_2)$$

$$90 = \tan^{-1}(\omega_{pc} T_1) + \tan^{-1}(\omega_{pc} T_2)$$

$$\tan^{-1}\left(\frac{\omega_{pc} T_1 + \omega_{pc} T_2}{1 - \omega_{pc}^2 T_1 T_2}\right) = 90$$

$$1 - \omega_{pc}^2 T_1 T_2 = 0$$

$$\omega_{pc} = \frac{1}{\sqrt{T_1 T_2}}$$

End of Solution

Q.26 Consider a system with input $x(t)$ and output $y(t) = x(e^t)$. The system is

- | | |
|-------------------------------|-----------------------------------|
| (a) Causal and time invariant | (b) Non-causal and time varying |
| (c) Causal and time varying | (d) Non-causal and time invariant |

[1 Mark : MCQ]

Ans. (b)

We have, $y(t) = x(e^t)$

At $t = 0$

$$y(0) = x(1)$$

i.e. present value of output depends on future value of input, hence it is non-causal.

For Time Variant:

Delay the input,

$$y(t) = x(e^t - t_o) \quad \dots(i)$$

Delay the output,

$$y(t - t_o) = x(e^{t-t_o}) \quad \dots(ii)$$

i.e. equations (i) \neq (ii)

Hence, it is time variant system.


End of Solution

- Q.27** Let $m(t)$ be a strictly band-limited signal with bandwidth B and energy E . Assuming $\omega_0 = 10B$, the energy in the signal $m(t)\cos\omega_0 t$ is dsbsv

- | | |
|-------------------|-------------------|
| (a) $\frac{E}{4}$ | (b) $\frac{E}{2}$ |
| (c) E | (d) $2E$ |

[1 Mark : MCQ]

Ans. (b)

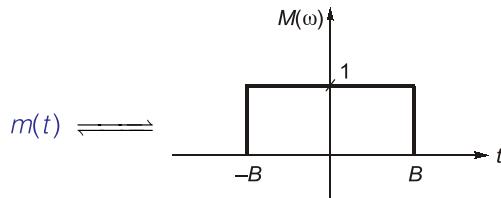

$$\text{Energy } (E) = \frac{1}{2\pi} \int_{-B}^{B} (1)^2 \cdot d\omega$$

$$E = \frac{B}{\pi}$$


Now, let

$$y(t) = m(t) \cos \omega_0 t$$

$$Y(\omega) = \frac{1}{2} [M(\omega - \omega_0) + M(\omega + \omega_0)]$$

Here;

$$\omega_0 = 10B$$

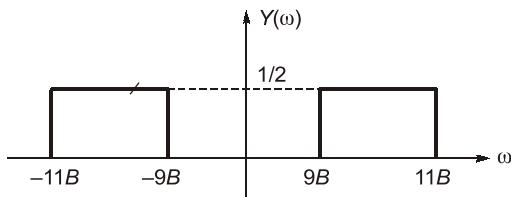

Now,

$$\text{Energy } (E') = \frac{1}{2\pi} \int_{-\infty}^{\infty} |Y(\omega)|^2 \cdot d\omega$$

$$= \frac{1}{2\pi} \left[\int_{-11B}^{-9B} \left(\frac{1}{2}\right)^2 \cdot d\omega + \int_{9B}^{11B} \left(\frac{1}{2}\right)^2 \cdot d\omega \right]$$

$$= \frac{1}{2\pi} \left[\frac{1}{4} \times 2B + \frac{1}{4} \times 2B \right]$$

$$E' = \frac{B}{2\pi} = \frac{1}{2} \left(\frac{B}{\pi} \right) = \frac{E}{2}$$

End of Solution

Q.28 The Fourier transform $X(\omega)$ of $x(t) = e^{-t^2}$ is

Note: $\int_{-\infty}^{\infty} e^{-y^2} dy = \sqrt{\pi}$

(a) $\sqrt{\pi} e^{-\frac{\omega^2}{2}}$

(b) $\frac{e^{-\frac{\omega^2}{4}}}{2\sqrt{\pi}}$

(c) $\sqrt{\pi} e^{-\frac{\omega^2}{4}}$

(d) $\sqrt{\pi} e^{-\frac{\omega^2}{2}}$

~~~

[1 Mark : MCQ]

**Ans.** (c)

We know:  $e^{-at^2}; a > 0 \xrightarrow{FT} \sqrt{\frac{\pi}{a}} \cdot e^{-\omega^2/4a}$

Here;  $a = 1$

$\therefore X(\omega) = \sqrt{\pi} \cdot e^{-\omega^2/4}$

**End of Solution**

**Q.29** In the table shown below, match the signal type with its spectral characteristics.

| Signal type                                                                                        | Spectral Characteristics  |
|----------------------------------------------------------------------------------------------------|---------------------------|
| (i) Continuous, aperiodic                                                                          | (a) Continuous, aperiodic |
| (ii) Continuous, periodic                                                                          | (b) Continuous, periodic  |
| (iii) Discrete, aperiodic                                                                          | (c) Discrete, aperiodic   |
| (iv) Discrete, periodic                                                                            | (d) Discrete, periodic    |
| (a) (i) $\rightarrow$ (a), (ii) $\rightarrow$ (b), (iii) $\rightarrow$ (c), (iv) $\rightarrow$ (d) |                           |
| (b) (i) $\rightarrow$ (a), (ii) $\rightarrow$ (c), (iii) $\rightarrow$ (b), (iv) $\rightarrow$ (d) |                           |
| (c) (i) $\rightarrow$ (d), (ii) $\rightarrow$ (b), (iii) $\rightarrow$ (c), (iv) $\rightarrow$ (a) |                           |
| (d) (i) $\rightarrow$ (a), (ii) $\rightarrow$ (c), (iii) $\rightarrow$ (d), (iv) $\rightarrow$ (b) |                           |

[1 Mark : MCQ]



# Rank Improvement Course for GATE 2024

**Commencing from**  
1<sup>st</sup> May, 2023

**Teaching Hours :**  
300 to 350 hours

**Course Validity :**  
Till GATE 2024 Exam

**LIVE-ONLINE  
COURSE**  
**Streams :**  
CE, ME, EE, EC, CS

## Key Features

- ✓ Comprehensive problem-solving sessions by India's top faculties.
- ✓ Focus on improving accuracy & speed.
- ✓ Practice all types of questions to brush up on your concepts.
- ✓ Newly develop workbooks (e-copy) in line with recent trends in GATE.
- ✓ Highly useful for repeaters candidates.

**Download  
the App**



Android



iOS

📞 9021300500

🌐 [www.madeeasyprime.com](http://www.madeeasyprime.com)


Ans. (b)

| Signal Types               | Spectral Characteristics   |
|----------------------------|----------------------------|
| • Continuous and aperiodic | • Aperiodic and continuous |
| • Continuous and periodic  | • Aperiodic and discrete   |
| • Discrete and aperiodic   | • Periodic and continuous  |
| • Discrete and periodic    | • Periodic and discrete    |


End of Solution

Q.30 For a real signal, which of the following is/are valid power spectral density/densities?

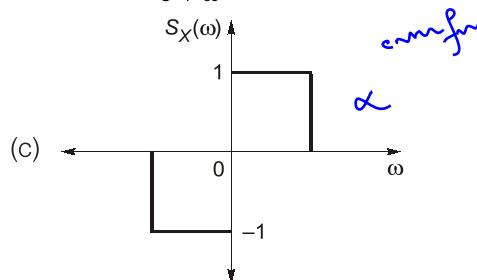(a)  $S_X(\omega) = \frac{2}{9 + \omega^2}$



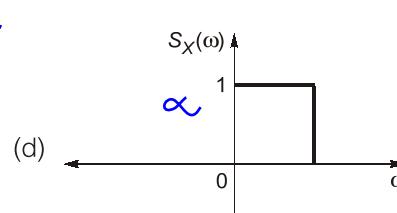(b)  $S_X(\omega) = e^{-\omega^2} \cos^2 \omega$



[1 Mark : MSQ]

Ans. (a, b)

(i)  $S_x(\omega) \geq 0$

(ii)  $S_x(\omega)$  is even function

Hence, options (a) and (b) are valid power spectral densities.

End of Solution

Q.31 The signal-to-noise ratio (SNR) of an ADC with a full-scale sinusoidal input is given to be 61.96 dB. The resolution of the ADC is \_\_\_\_ bits. (rounded off to the nearest integer).

[1 Mark : NAT]

Ans. (10)

We know that for sinusoidal input, the signal to noise ratio (SNR) is given as,

$$\text{SNR} = 1.76 + 6.02 n \text{ dB}$$


$$61.96 \text{ dB} = 1.76 + 6.02 n \text{ dB}$$

$$6.02 n = 61.96 - 1.76$$

$$\therefore n = 10 \text{ bits}$$


End of Solution

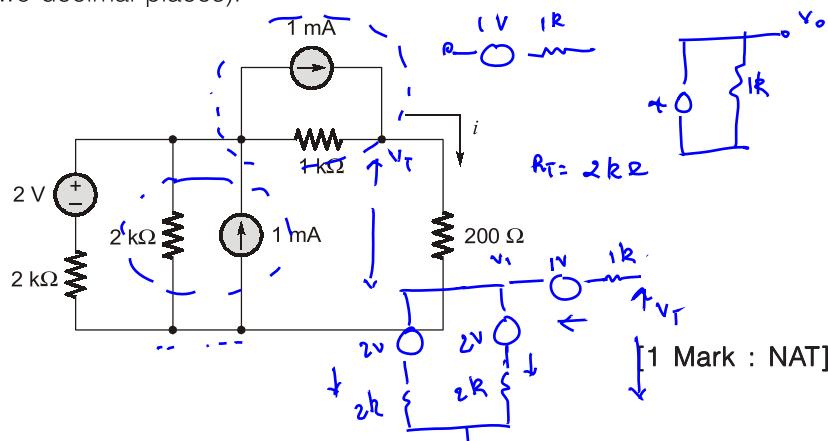- Q.32** In the circuit shown below, the current  $i$  flowing through  $200\ \Omega$  resistor is \_\_\_\_\_ mA.  
 (rounded off to two decimal places).



**Ans.** (1.36)

By applying source transformation,

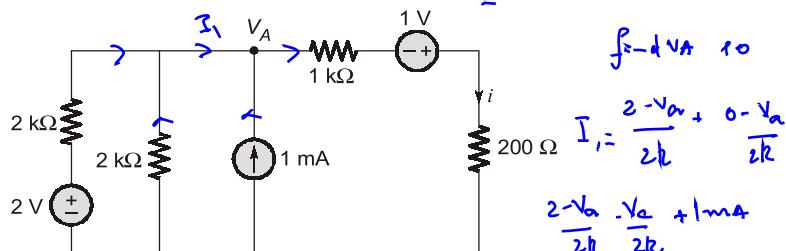

Apply nodal at node  $V_A$ ,

$$\frac{V_A - 2}{2k} + \frac{V_A}{2k} + \frac{V_A + 1}{1.2k} = 1\text{ mA}$$

$$V_A \left[ \frac{1}{2} + \frac{1}{2} + \frac{1}{1.2} \right] = 1 + \frac{2}{2} - \left( \frac{1}{1.2} \right)$$

$$V_A = 0.636\text{ V}$$

The current through  $200\ \Omega$  resistor,

$$i = \frac{V_A + 1}{1.2k} = \frac{0.636 + 1}{1.2}$$

$$i = 1.36\text{ mA}$$

$$\frac{2 - V_A}{1k} = \frac{V_A + 1}{1.2k}$$

$$\frac{2 - V_A}{1.2k} = V_A \left( \frac{1}{1.2k} + \frac{1}{1k} \right)$$

$$\frac{2}{1.2k} = V_A \left( \frac{1}{1.2k} + \frac{1}{1k} \right)$$


$$i = \frac{V_A + 1}{1.2k} = 1.36\text{ mA}$$

**End of Solution**

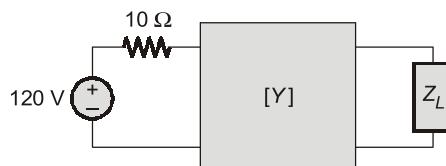- Q.33** For the two port network shown below, the [Y]-parameters is given as

$$[Y] = \frac{1}{100} \begin{bmatrix} 2 & -1 \\ -1 & 4/3 \end{bmatrix} S$$


The value of load impedance  $Z_L$ , in  $\Omega$ , for maximum power transfer will be \_\_\_\_\_.  
 (rounded off to the nearest integer).



[1 Mark : NAT]

**Ans. (80)**

$$[Y] = \begin{bmatrix} \frac{2}{100} & -\frac{1}{100} \\ -\frac{1}{100} & \frac{4}{300} \end{bmatrix}$$

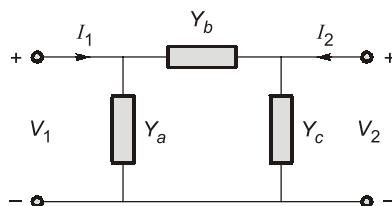 For the given  $Y$ -parameter the two-port network is


$$Y_{11} = Y_a + Y_b = \frac{2}{100}$$

$$Y_{12} = Y_{21} = -Y_b = -\frac{1}{100}$$

$$Y_{22} = Y_b + Y_c = \frac{4}{300}$$



On solving,

$$Y_b = \frac{1}{100} S$$

$$Y_a = \frac{1}{100} S$$

$$Y_c = \frac{1}{300} S$$

The network becomes,

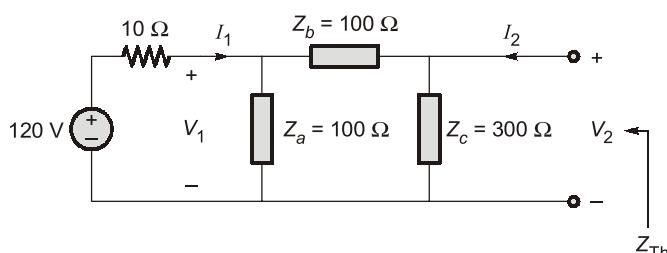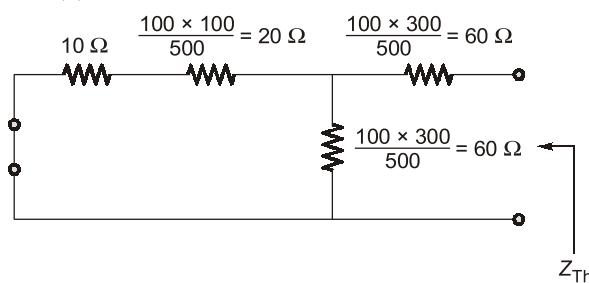
 Converting  $\Delta$  – to  $\lambda$ ,


$$Z_{Th} = 60 + [(20 + 10) \parallel 60]$$


$$= 60 + \frac{30 \times 60}{30 + 60} = 80 \Omega$$

For maximum power transfer,

$$Z_L = Z_{Th} = 80 \Omega$$

**End of Solution**

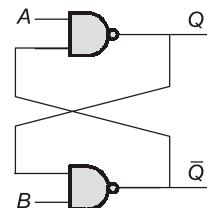
- Q.34** For the circuit shown below, the propagation delay of each NAND gate is 1 ns. The critical path delay, in ns, is \_\_\_\_\_ (rounded off to the nearest integer).



[1 Mark : NAT]

**Ans. (2)**


The given circuit can be drawn as;

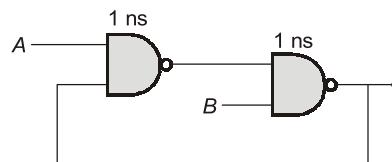

$$\begin{aligned}\therefore \text{The critical path delay} &= 1 \text{ ns} + 1 \text{ ns} \\ &= 2 \text{ ns}\end{aligned}$$

**End of Solution**

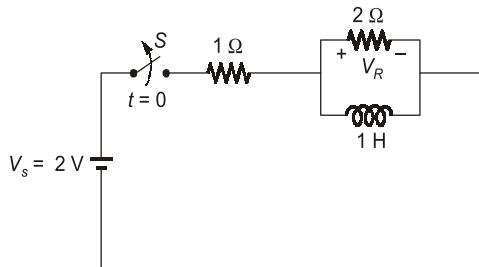
- Q.35** In the circuit shown below, switch  $S$  was closed for a long time. If the switch is opened at  $t = 0$ , the maximum magnitude of the voltage  $V_R$ , in volts, is \_\_\_\_\_ (rounded off to the nearest integer).




[1 Mark : NAT]

**Ans. (4)**

At  $t = 0^-$

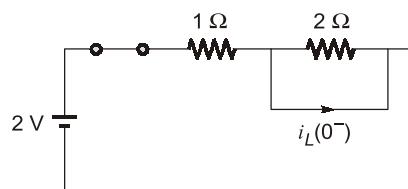

$$i_L(0^-) = \frac{2}{1} = 2 \text{ A}$$

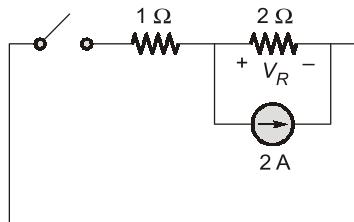 At  $t = 0^+$ 


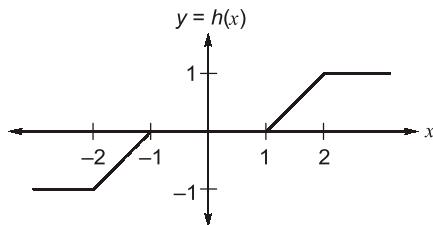
$$V_R = -2 \times 2 = -4$$

 Magnitude of voltage  $V_R$ ,

$$|V_R| = 4$$

**End of Solution**


- Q.36** A random variable  $X$ , distributed normally as  $N(0,1)$ , undergoes the transformation  $Y = h(X)$ , given in the figure. The form of the probability density function of  $Y$  is (In the options given below,  $a, b, c$  are non-zero constants and  $g(y)$  is piece-wise continuous function)



- (a)  $a\delta(y - 1) + b\delta(y + 1) + g(y)$
- (b)  $a\delta(y + 1) + b\delta(y) + c\delta(y - 1) + g(y)$
- (c)  $a\delta(y + 2) + b\delta(y) + c\delta(y - 2) + g(y)$
- (d)  $a\delta(y + 1) + b\delta(y - 2) + g(y)$

**[2 Marks : MCQ]**
**Ans. (b)**

$$X = N(0, 1)$$

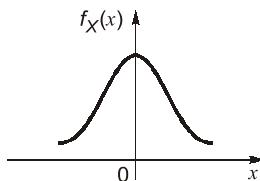

$$f_X(x) = \frac{1}{\sqrt{2\pi}} e^{-x^2/2}$$



# Live-Online Classes for SSC-JE 2023

Batches are live

Validity: Till 31<sup>st</sup> July, 2023

**TECHNICAL &  
NON-TECHNICAL  
SYLLABUS**


**Streams :**  
CE, ME, EE

## Course Details

| <b>CE<br/>Only Technical</b>   | <b>ME<br/>Only Technical</b>   | <b>EE<br/>Only Technical</b>   | <b>Non-Tech<br/>(RA + GS)</b>  |
|--------------------------------|--------------------------------|--------------------------------|--------------------------------|
| Teaching Hrs : <b>650 Hrs</b>  | Teaching Hrs : <b>450 Hrs</b>  | Teaching Hrs : <b>300 Hrs</b>  | Teaching Hrs : <b>260 Hrs</b>  |
| Total No. of Books : <b>16</b> | Total No. of Books : <b>15</b> | Total No. of Books : <b>10</b> | Total No. of Books : <b>03</b> |
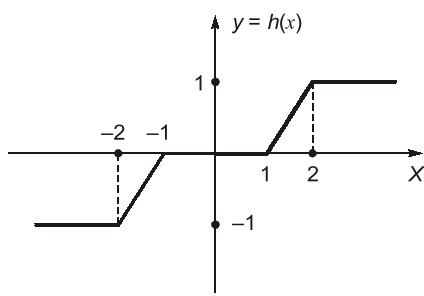
## Key Features

- ✓ Live Classes by experienced and renowned faculties having experience in SSC-JE field.
- ✓ Systematic subject sequence for Paper-I and Paper-II.
- ✓ Comprehensive coverage of Technical & Non-technical syllabus for Prelims & Mains.
- ✓ Well-researched study materials.
- ✓ Facility of watching video thrice, i.e., 1 Live session + 2 Recorded sessions.



$$\begin{aligned}
 Y &= -1 ; x \leq -2 \\
 &0 ; -1 \leq x \leq 1 \\
 &1 ; x \geq 2 \\
 &x + 1 ; -2 \leq x \leq -1 \\
 &x - 1 ; 1 \leq x \leq 2
 \end{aligned}$$

$Y$  is taking discrete set of values and a continuous range of values, so it is mixed random variable.

From the given options, density function of ' $Y$ ' will be.

$$f_Y(y) = a\delta(y + 1) + b\delta(y) + c\delta(y - 1) + g(y)$$

*wlc*

End of Solution

- Q.37** The value of the line integral  $\int_P^Q (z^2 dx + 3y^2 dy + 2xz dz)$  along the straight line joining the points  $P(1, 1, 2)$  and  $Q(2, 3, 1)$  is
- (a) 20                          (b) 24  
 (c) 29                          (d) -5

[2 Marks : MCQ]

**Ans.** (b)

$\int_P^Q z^2 dx + 3y^2 dy + 2xz dz$  along the line joining the points  $P(1, 1, 2)$  and  $Q(2, 3, 1)$  is

$$\begin{aligned}
 &= \int_{P(1,2)}^{P(2,1)} z^2 dx + 2xy dz + \int_{y=1}^3 3y^2 dy \\
 &= (xz^2)_{(1,2)}^{(2,1)} + (y^3)_1^3 \\
 &= (2 \times 1^2 - 1 \times 2^2) + (3^3 - 1^3) \\
 &= -2 + 26 = 24
 \end{aligned}$$

End of Solution

**Q.38** Let  $x$  be an  $n \times 1$  real column vector with length  $l = \sqrt{x^T x}$ . The trace of the matrix  $P = xx^T$  is

(a)  $l^2$

(c)  $l$

(b)  $\frac{l^2}{4}$

(d)  $\frac{l^2}{2}$

**[2 Marks : MCQ]**
**Ans. (a)**

Given,

$$l = \sqrt{x^T x}, P = (xx^T)_{n \times n}$$

Let

$$(x)_{n \times 1} = \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ \vdots \\ \vdots \\ x_n \end{bmatrix}$$

$$l = \sqrt{x^T x} = \sqrt{x_1^2 + x_2^2 + x_3^2 + \dots + x_n^2}$$

$$P = xx^T$$


$$= \begin{bmatrix} x_1 \\ x_2 \\ x_3 \\ \vdots \\ \vdots \\ x_n \end{bmatrix} [x_1 \ x_2 \ x_3 \ \dots \ x_n]$$

$$P = \begin{bmatrix} x_1^2 & & & \\ & x_1^2 & & \\ & & - & \\ & & & - \\ & & & x_n^2 \end{bmatrix}$$

$$\text{Trace of } P = x_1^2 + x_2^2 + \dots + x_n^2 = l^2$$

**End of Solution**

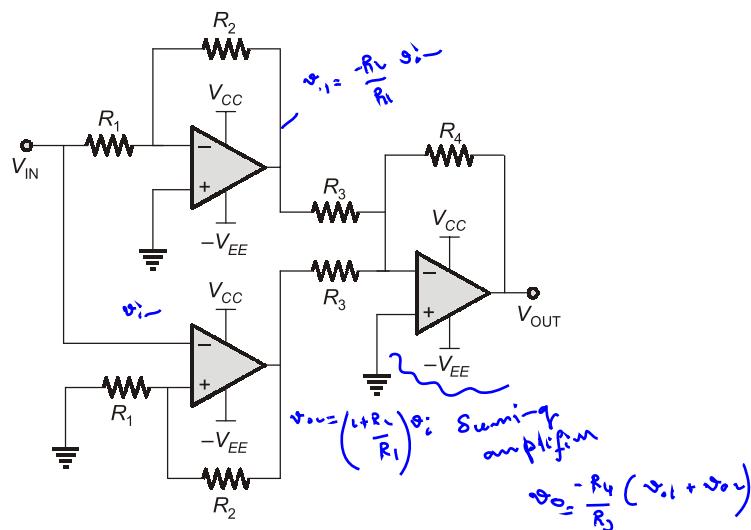**Q.39** The  $\frac{V_{\text{OUT}}}{V_{\text{IN}}}$  of the circuit shown below is



(a)  $-\frac{R_4}{R_3}$


(b)  $\frac{R_4}{R_3}$

(c)  $1 + \frac{R_4}{R_3}$

(d)  $1 - \frac{R_4}{R_3}$

[2 Marks : MCQ]

**Ans. (a)**

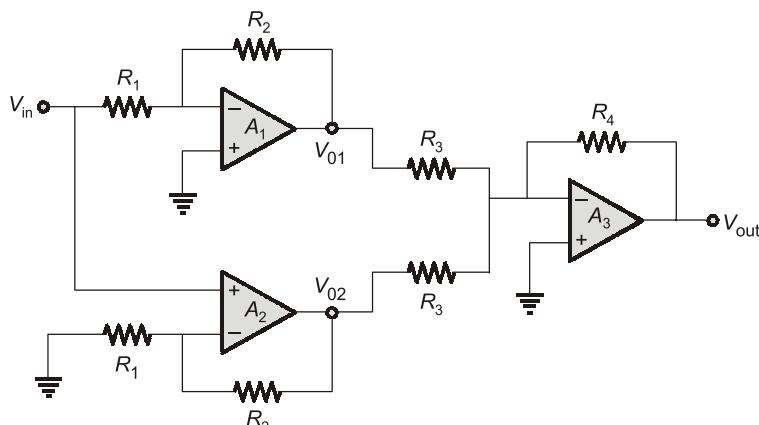

Here,  $A_1$  is an inverting amplifier and  $A_2$  is a non-inverting amplifier.

$$V_{01} = \frac{-R_2}{R_1} V_{\text{in}}$$

$$V_{02} = \left(1 + \frac{R_2}{R_1}\right) V_{\text{in}}$$

Also,  $A_3$  is an inverting summing amplifier,



$$V_{\text{out}} = \frac{-R_4}{R_3} V_{01} - \frac{R_4}{R_3} V_{02} = \frac{-R_4}{R_3} \left[ \frac{R_2}{R_1} V_{in} + \left( 1 + \frac{R_2}{R_1} \right) V_{in} \right]$$

$$V_{\text{out}} = \frac{-R_4}{R_3} V_{in}$$

$$\text{Gain, } \frac{V_{\text{out}}}{V_{in}} = \frac{-R_4}{R_3}$$

**End of Solution**

- Q.40** In the circuit shown below,  $D_1$  and  $D_2$  are silicon diodes with cut-in voltage of 0.7 V.  $V_{in}$  and  $V_{out}$  are input and output voltages in volts. The transfer characteristic is

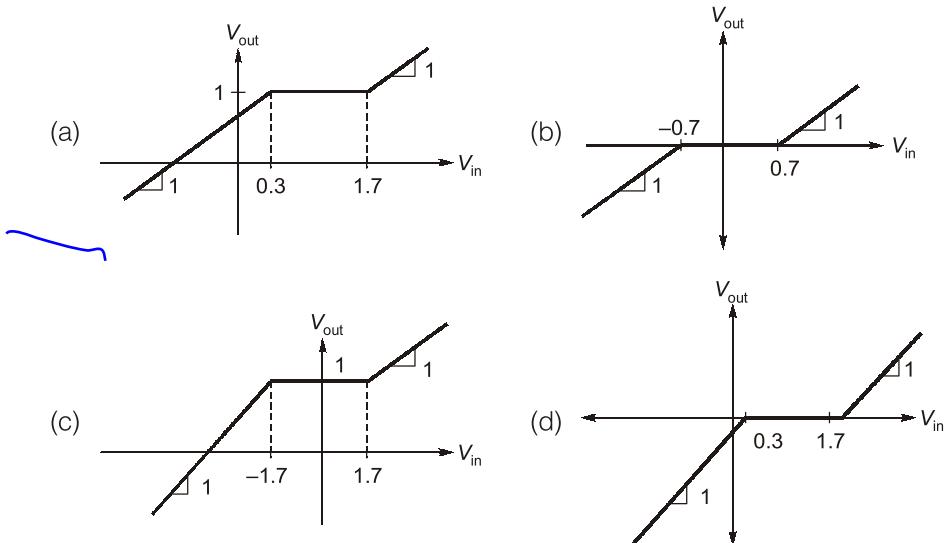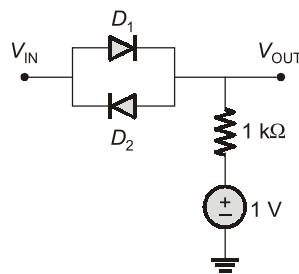
**[2 Marks : MCQ]**
**Ans. (a)**
**Case I:**

$$V_g = 0.7 \text{ V}$$

 For the +ve half cycle if input  $V_{in}$ ,

 $D_1 \rightarrow \text{ON} \text{ and } D_2 \rightarrow \text{OFF}$ 

 For diode  $D_1$ :  $V_{in} - 1 \text{ V} > 0.7$ 

$$V_{in} > 1.7 \text{ V}$$

$$V_o = V_{in} - 0.7$$

**Case II:**

 For the +ve half cycle if input  $V_{in}$ ,

 $D_1 \rightarrow \text{OFF}$  and  $D_2 \rightarrow \text{ON}$ 

 For diode  $D_2$ :  $1 - V_{in} > 0.7$ 

$$V_{in} < 0.3V$$

$$V_0 = V_{in} + 0.7$$


**Case III:**

$$0.3V < V_{in} < 1.7V$$


 $D_1 \rightarrow \text{OFF}$  and  $D_2 \rightarrow \text{OFF}$ 

$$V_0 = 1V$$

Transfer characteristics,

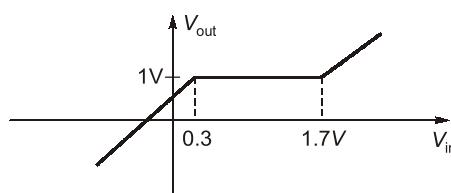
**End of Solution**

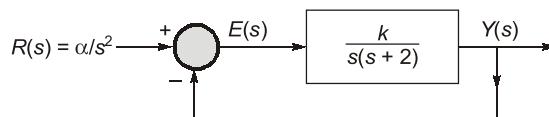- Q.41** A closed loop system is shown in the figure where  $k > 0$  and  $\alpha > 0$ . The steady state error due to a ramp input ( $R(s) = \alpha/s^2$ ) is given by



(a)  $\frac{2\alpha}{k}$

(c)  $\frac{\alpha}{2k}$

(b)  $\frac{\alpha}{k}$

(d)  $\frac{\alpha}{4k}$

**[2 Marks : MCQ]**
**Ans. (a)**

 Given, input is  $r(t) = \alpha t u(t)$ 

$$R(s) = \frac{\alpha}{s^2}$$

From the figure,

$$G(s)H(s) = \frac{K}{s(s+2)}$$

Now steady state error for Ramp input is

$$e_{ss} = \frac{\alpha}{K_v}, \text{ where } \alpha \text{ is the magnitude of Ramp input}$$

$$K_v = \lim_{s \rightarrow 0} [sG(s)H(s)]$$

$$K_v = \lim_{s \rightarrow 0} \left[ \frac{s \times K}{s(s+2)} \right] = \frac{K}{2}$$



# Live-Online Course for General Studies for State Engineering and SSC Exams

FULL  
FLEDGED  
COURSE FOR  
GENERAL  
STUDIES

**Subject Covered :** History, General Science, Polity, Environment, Geography, General Knowledge, Economy & Current Affairs

**Duration :** 3 Months | **Validity :** 6 Months  
Batches commencing from **22<sup>nd</sup> Feb, 2023**

## Key Features


- ✓ 250 Hrs of quality teaching by renowned teachers of MADE EASY.
- ✓ Printed study material will be dispatched to your address.
- ✓ Comprehensive coverage as per latest syllabus and trends of various competitive exams.

$$\therefore e_{ss} = \frac{\alpha \times 2}{K}$$

$$e_{ss} = \frac{2\alpha}{K}$$

**End of Solution**

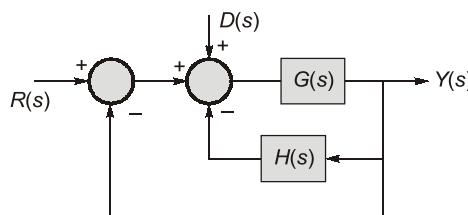- Q.42** In the following block diagram,  $R(s)$  and  $D(s)$  are two inputs. The output  $Y(s)$  is expressed as  $Y(s) = G_1(s)R(s) + G_2(s)D(s)$ .  
 $G_1(s)$  and  $G_2(s)$  are given by




(a)  ~~$G_1(s) = \frac{G(s)}{1+G(s)+G(s)H(s)}$~~  and  $G_2(s) = \frac{G(s)}{1+G(s)+G(s)H(s)}$


(b)  $G_1(s) = \frac{G(s)}{1+G(s)+H(s)}$  and  $G_2(s) = \frac{G(s)}{1+G(s)+H(s)}$


(c)  $G_1(s) = \frac{G(s)}{1+G(s)+H(s)}$  and  $G_2(s) = \frac{G(s)}{1+G(s)+G(s)H(s)}$

(d)  $G_1(s) = \frac{G(s)}{1+G(s)+G(s)H(s)}$  and  $G_2(s) = \frac{G(s)}{1+G(s)+H(s)}$

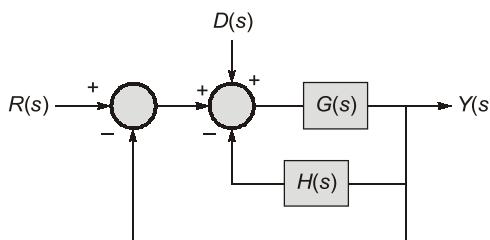**[2 Marks : MCQ]**
**Ans. (a)**


$$Y(s) = \underbrace{\frac{G_1(s)R(s)}{Y_1(s)}} + \underbrace{\frac{G_2(s)D(s)}{Y_2(s)}}$$

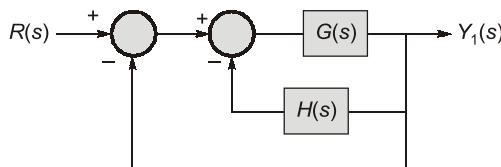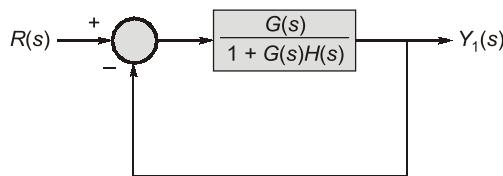 Considering first  $R(s)$  only, then  $Y(s)$  is  $Y_1(s)$ 




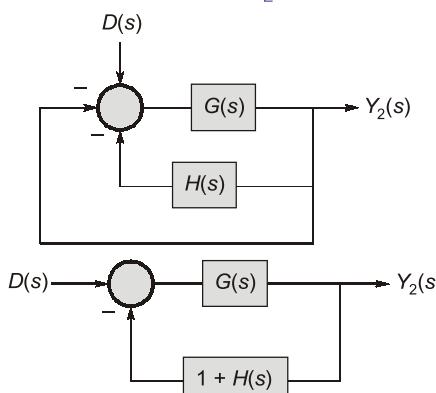
$$\frac{Y_1(s)}{R(s)} = \frac{\frac{G(s)}{1+G(s)H(s)}}{1 + \frac{G(s)}{1+G(s)H(s)}}$$

$$\frac{Y_1(s)}{R(s)} = \frac{G(s)}{1+G(s)H(s)+G(s)}$$

$$Y_1(s) = \left[ \frac{G(s)}{1+G(s)+G(s)H(s)} \right] R(s)$$

$$\therefore G_1(s) = \frac{G(s)}{1+G(s)+G(s)H(s)}$$

Now considering  $D(s)$  only, then  $Y(s)$  is  $Y_2(s)$



$$\frac{Y_2(s)}{D(s)} = \frac{G(s)}{1+G(s)[1+H(s)]}$$

$$Y_2(s) = \left[ \frac{G(s)}{1+G(s)+G(s)H(s)} \right] D(s)$$

$$\therefore G_2(s) = \frac{G(s)}{1+G(s)+G(s)H(s)}$$

Hence,  $G_1(s)$  and  $G_2(s)$  both are equal.

**End of Solution**

**Q.43** The state equation of a second order system is

$\dot{x}(t) = Ax(t)$ ,  $x(0)$  is the initial condition.

Suppose  $\lambda_1$  and  $\lambda_2$  are two distinct eigenvalues of  $A$  and  $v_1$  and  $v_2$  are the corresponding eigenvectors. For constants  $\alpha_1$  and  $\alpha_2$ , the solution,  $x(t)$ , of the state equation is

(a)  $\sum_{i=1}^2 \alpha_i e^{\lambda_i t} v_i$

(b)  $\sum_{i=1}^2 \alpha_i e^{2\lambda_i t} v_i$

(c)  $\sum_{i=1}^2 \alpha_i e^{3\lambda_i t} v_i$


(d)  $\sum_{i=1}^2 \alpha_i e^{4\lambda_i t} v_i$

[2 Marks : MCQ]

**Ans. (a)**

**End of Solution**

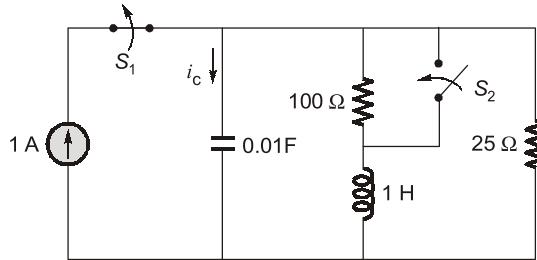**Q.44** The switch  $S_1$  was closed and  $S_2$  was open for a long time. At  $t = 0$ , switch  $S_1$  is opened and  $S_2$  is closed, simultaneously. The value of  $i_c(0^+)$ , in amperes, is




- (a) 1  
(c) 0.2

- (b) -1  
(d) 0.8

[2 Marks : MCQ]

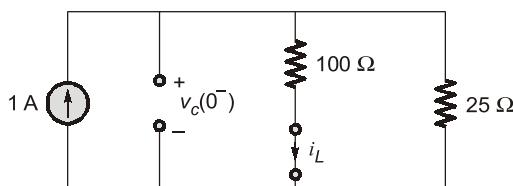**Ans. (b)**


At  $t = 0^-$ ;  $S_1 \rightarrow$  closed,  $S_2 \rightarrow$  opened



$$i_L(0^-) = \frac{1 \times 25}{100 + 25} = 0.2 \text{ A}$$

$$v_c(0^-) = \frac{1}{5} \times 100 = 20 \text{ V}$$

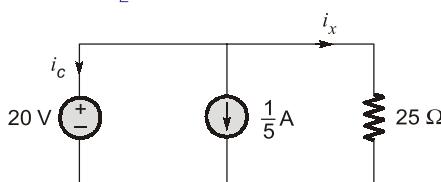At  $t = 0^+$ ;  $S_1 \rightarrow$  opened,  $S_2 \rightarrow$  closed



$$i_x = \frac{20}{25} = \frac{4}{5} A = 0.8 A$$

By KCL:

$$-i_c = i_x + 0.2 = 0.8 + 0.2$$

$$i_c = -1 A$$

**End of Solution**

**Q.45** Let a frequency modulated (FM) signal

$x(t) = A \cos(\omega_c t + k_f \int_{-\infty}^t m(\lambda) d\lambda)$ , where  $m(t)$  is a message signal of bandwidth  $W$ . It is passed through a non-linear system with output  $y(t) = 2x(t) + 5(x(t))^2$ . Let  $B_T$  denote the FM bandwidth. The minimum value of  $\omega_c$  required to recover  $x(t)$  from  $y(t)$  is

(a)  $B_T + W$

(b)  $\frac{3}{2}B_T$

(c)  $2B_T + W$


(d)  $\frac{5}{2}B_T$

**[2 Marks : MCQ]**


Ans. (b)

$$x(t) = A \cos \left[ \omega_c t + K_f \int_{-\infty}^t m(\lambda) d\lambda \right]$$
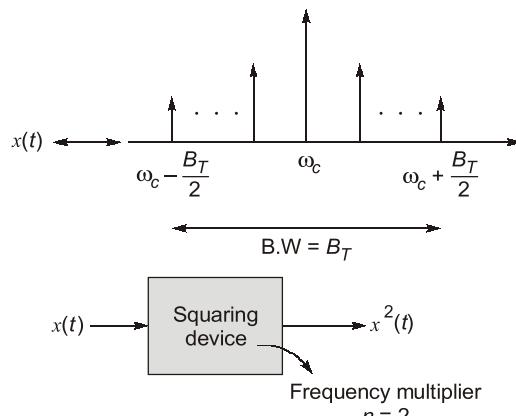
$$B.W. [x(t)] \rightarrow BT = 2[\Delta f + \omega]$$



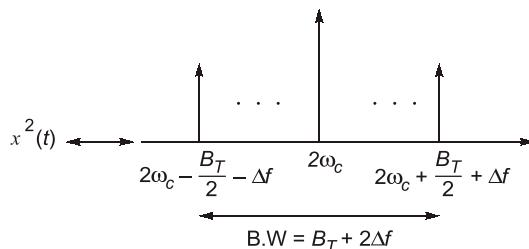
$$x^2(t) \rightarrow \begin{cases} \Delta f' = 2\Delta f \\ \omega'_c = 2\omega_c \end{cases}$$



$$\begin{aligned} BW[x^2(t)] &= 2[\Delta f' + \omega] \\ &= 2[2\Delta f + \omega] = BT + 2\Delta f \end{aligned}$$

$$y(t) = 2x(t) + 5x^2(t)$$

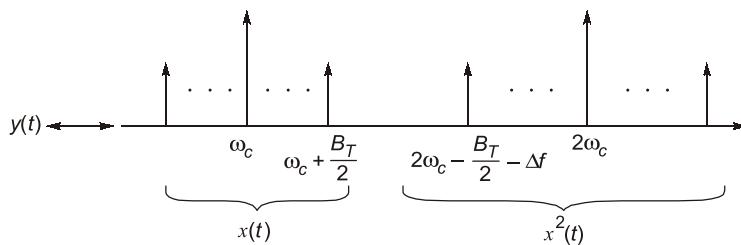

To recover  $x(t) \rightarrow 2\omega_c - \frac{B_T}{2} - \Delta f > \omega_c + \frac{B_T}{2}$

$$\omega_c > \Delta f + BT$$

$$\omega_c > \Delta f + 2\Delta f + 2\omega$$

$$\omega_c > 3\Delta f + 2\omega$$

$$\omega_c > \frac{3}{2} \{2[\Delta f + \omega]\} - \omega$$

$$\omega_c > \frac{3}{2} B_T - \omega$$

Compared to FM BW, message BW is very small. So, that it can be ignored.


$$\omega_c > \frac{3}{2} B_T$$

$$[\omega_c]_{\min} = \frac{3}{2} B_T$$

**End of Solution**

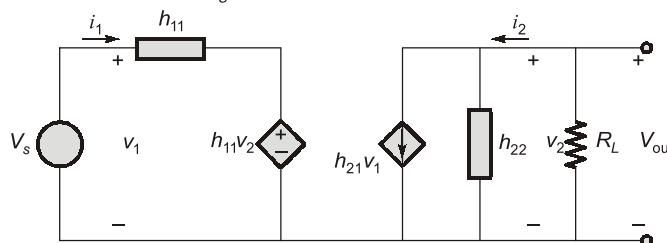**Q.46** The h-parameters of a two port network are shown below. The condition for the maximum

small signal voltage gain  $\frac{V_{out}}{V_s}$  is



- (a)  $h_{11} = 0$ ,  $h_{12} = 0$ ,  $h_{21} = \text{very high}$  and  $h_{22} = 0$
- (b)  $h_{11} = \text{very high}$ ,  $h_{12} = 0$ ,  $h_{21} = \text{very high}$  and  $h_{22} = 0$
- (c)  $h_{11} = 0$ ,  $h_{12} = \text{very high}$ ,  $h_{21} = \text{very high}$  and  $h_{22} = 0$
- (d)  $h_{11} = 0$ ,  $h_{12} = 0$ ,  $h_{21} = \text{very high}$  and  $h_{22} = \text{very high}$

**[2 Marks : MCQ]**

Ans. (\*)

Dependent current source should have  $h_{21} I_1$  instead of  $h_{21} V_1$  according to  $h$ -parameter.

$$A_v = \frac{V_{out}}{V_s} = \frac{-h_{21} I_1 \times \left( \frac{1}{h_{22}} \parallel R_L \right)}{h_{11} I_1 + h_{12} V_2}$$

To achieve maximum  $\frac{V_{out}}{V_s}$ ,

$$\begin{aligned} h_{11} &= 0, \quad h_{12} = 0 \\ h_{21} &= \text{Very high}, \quad h_{22} = 0 \end{aligned}$$

Hence, answer should be (a) according to  $h_{21} I_1$ .

**End of Solution**

- Q.47** Consider a discrete-time periodic signal with period  $N = 5$ . Let the discrete-time Fourier series (DTFS) representation be  $x[n] = \sum_{k=0}^4 a_k e^{\frac{j k 2\pi n}{5}}$ , where  $a_0 = 1$ ,  $a_1 = 3j$ ,  $a_2 = 2j$ ,  $a_3 = -2j$  and  $a_4 = -3j$ . The value of the sum  $\sum_{n=0}^4 x[n] \sin \frac{4\pi n}{5}$  is
- (a) -10      (b) 10  
 (c) -2      (d) 2

[2 Marks : MCQ]

Ans. (a)

$$\begin{aligned} \text{Let, } I &= \sum_{n=0}^4 x(n) \sin \frac{4\pi n}{5} \\ &= \frac{1}{2j} \sum_{n=0}^4 x(n) \cdot \left[ e^{\frac{j 4\pi n}{5}} - e^{-\frac{j 4\pi n}{5}} \right] \\ &= \frac{1}{2j} \left[ \sum_{n=0}^4 x(n) e^{\frac{j 4\pi n}{5}} - \sum_{n=0}^4 x(n) \cdot e^{-\frac{j 4\pi n}{5}} \right] \quad \dots(i) \end{aligned}$$

$$\begin{aligned} \text{As we know, } a_k &= \frac{1}{N} \sum_{n=0}^4 x(n) \cdot e^{-jk \cdot \frac{2\pi}{N} n} \\ &= \frac{1}{5} \sum_{n=0}^4 x(n) \cdot e^{-j \frac{2\pi}{5} kn} \end{aligned}$$

$$\text{Put } K = 2 ; \quad a_2 = \frac{1}{5} \sum_{n=0}^4 x(n) \cdot e^{-j \frac{4\pi n}{5}}$$

$$\text{Put } K = -2 ; \quad a_{-2} = \frac{1}{5} \sum_{n=0}^4 x(n) \cdot e^{j \frac{4\pi n}{5}}$$

$$\text{From equation (i), } I = \frac{1}{2j} [5a_{-2} - 5a_2]$$

$$= \frac{5}{2j} [a_3 - a_2]$$

$$\left[ \begin{array}{l} a_{-2} = a_{-2+N} \\ \therefore = a_{-2+5} \\ = a_3 \end{array} \right]$$

$$\Rightarrow I = \frac{5}{2j} [-2j - 2j] = -10$$

**End of Solution**

**Q.48** Let an input  $x[n]$  having discrete time Fourier transform.

$X(e^{j\Omega}) = 1 - e^{-j\Omega} + 2e^{-3j\Omega}$  be passed through an LTI system. The frequency response of the LTI system is  $H(e^{j\Omega}) = 1 - \frac{1}{2}e^{-j2\Omega}$ . The output  $y[n]$  of the system is

- (a)  $\delta[n] + \delta[n-1] - \frac{1}{2}\delta[n-2] - \frac{5}{2}\delta[n-3] + \delta[n-5]$
- (b)  $\delta[n] - \delta[n-1] - \frac{1}{2}\delta[n-2] - \frac{5}{2}\delta[n-3] + \delta[n-5]$
- (c)  $\delta[n] - \delta[n-1] - \frac{1}{2}\delta[n-2] + \frac{5}{2}\delta[n-3] - \delta[n-5]$
- (d)  $\delta[n] + \delta[n-1] + \frac{1}{2}\delta[n-2] + \frac{5}{2}\delta[n-3] + \delta[n-5]$

**[2 Marks : MCQ]**

**Ans. (c)**

$$y[n] = x[n] * h[n]$$

$$Y(e^{j\Omega}) = X(e^{j\Omega})H(e^{j\Omega})$$

$$= \left[ 1 - e^{-j\Omega} + 2e^{-3j\Omega} \right] \left[ 1 - \frac{1}{2}e^{-j2\Omega} \right]$$

$$= 1 - e^{-j\Omega} + 2.5e^{-3j\Omega} - 0.5e^{-j2\Omega} - e^{-j5\Omega}$$

Taking IDTFT;

$$y[n] = \delta[n] - \delta[n-1] - 0.5\delta[n-2] + 2.5\delta[n-3] - \delta[n-5]$$

**End of Solution**

**Q.49** Let  $x(t) = 10 \cos(10.5Wt)$  be passed through an LTI system having impulse response


$$h(t) = \pi \left( \frac{\sin Wt}{\pi t} \right)^2 \cos 10Wt$$

- (a)  $\left( \frac{15W}{4} \right) \cos(10.5Wt)$
- (b)  $\left( \frac{15W}{2} \right) \cos(10.5Wt)$
- (c)  $\left( \frac{15W}{8} \right) \cos(10.5Wt)$
- (d)  $(15W) \cos(10.5Wt)$

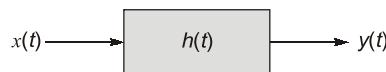**[2 Marks : MCQ]**

Ans. (a)

Given  $h(t)$  is Real and Even. When sinusoidal input applied to LTI system having even impulse response, then output will also be sinusoidal.



here,


$$y(t) = H(W)|_{W=10.5W} \cdot 10\cos(10.5Wt)$$

let,

$$h(t) = f(t)\cos 10Wt$$


where,
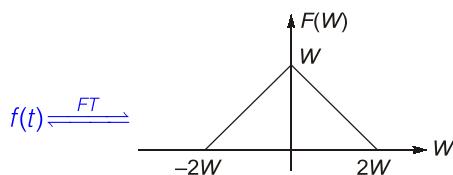
$$f(t) = \pi \left( \frac{\sin Wt}{\pi t} \right)^2$$



Now;
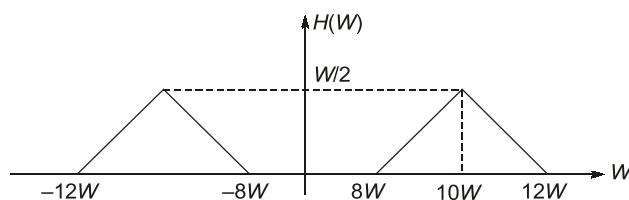
$$H(W) = \frac{1}{2} [F(W + 10W) + F(W - 10W)]$$




$$\therefore H(W)|_{W=10.5W} = \frac{3}{8}W$$

Hence,

$$\begin{aligned} y(t) &= \left( \frac{3}{8}W \right) (10\cos 10.5Wt) \\ &= \frac{15}{4}W \cos 10.5Wt \end{aligned}$$

End of Solution

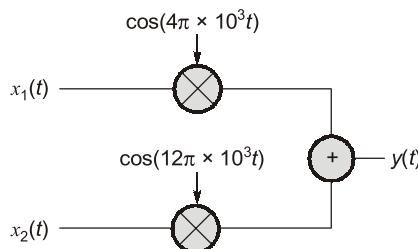**Q.50** Let  $x_1(t)$  and  $x_2(t)$  be two band-limited signals having bandwidth  $B = 4\pi \times 10^3$  rad/s each. In the figure below, the Nyquist sampling frequency, in rad/s, required to sample  $y(t)$ , is




- (a)  $20\pi \times 10^3$   
(c)  $8\pi \times 10^3$

- (b)  $40\pi \times 10^3$   
(d)  $32\pi \times 10^3$

[2 Marks : MCQ]

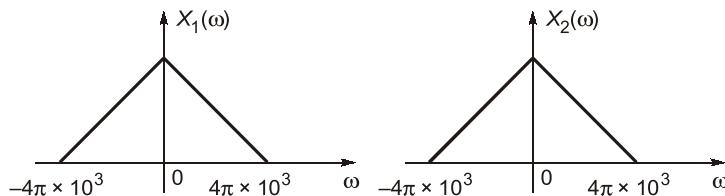
**Ans. (d)**

Given that,  $x_1(t)$  and  $x_2(t)$  are two bandlimited signals having bandwidth  $B = 4\pi \times 10^3$  rad/sec.



and
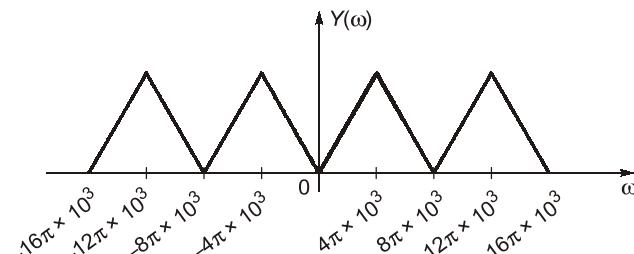
$$y(t) = x_2(t)\cos(12\pi \times 10^3 t) + x_1(t) \cos(4\pi \times 10^3 t)$$




So,

$$\begin{aligned} \text{Nyquist rate} &= 2\omega_{\max} \\ &= 2[16\pi \times 10^3] \\ &= 32\pi \times 10^3 \text{ rad/sec} \end{aligned}$$

**End of Solution**
**Q.51** The S-parameters of a two port network is given as

$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

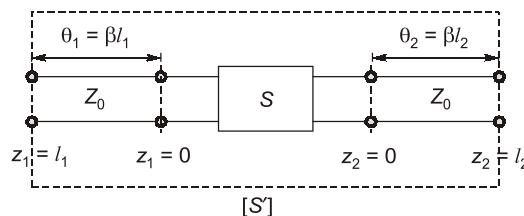with reference to  $Z_0$ . Two lossless transmission line sections of electrical lengths  $\theta_1 = \beta l_1$  and  $\theta_2 = \beta l_2$  are added to the input and output ports for measurement purposes, respectively. The S-parameters  $[S']$  of the resultant two port network is



$$(a) \begin{bmatrix} S_{11}e^{-j2\theta_1} & S_{12}e^{-j(\theta_1+\theta_2)} \\ S_{21}e^{-j(\theta_1+\theta_2)} & S_{22}e^{-j2\theta_2} \end{bmatrix}$$


$$(b) \begin{bmatrix} S_{11}e^{j2\theta_1} & S_{12}e^{-j(\theta_1+\theta_2)} \\ S_{21}e^{-j(\theta_1+\theta_2)} & S_{22}e^{j2\theta_2} \end{bmatrix}$$

$$(c) \begin{bmatrix} S_{11}e^{j2\theta_1} & S_{12}e^{j(\theta_1+\theta_2)} \\ S_{21}e^{j(\theta_1+\theta_2)} & S_{22}e^{j2\theta_2} \end{bmatrix}$$

$$(d) \begin{bmatrix} S_{11}e^{-j2\theta_1} & S_{12}e^{j(\theta_1+\theta_2)} \\ S_{21}e^{j(\theta_1+\theta_2)} & S_{22}e^{-j2\theta_2} \end{bmatrix}$$

**[2 Marks : MCQ]**

**Ans. (a)**

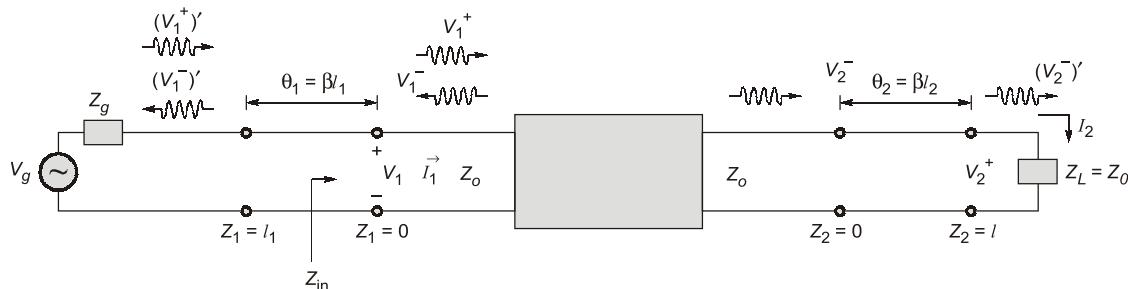 Let us evaluate  $S_{11}$  and  $S_{21}$  first at  $V_2^+ = 0$ 

**(a)  $S_{11}$  :**

$$V_1 = V_1^+ + V_1^- = (V_1^+)' e^{-j\beta l_1} + (V_1^-)' e^{+j\beta l_1}$$

$$\therefore V_1^+ = (V_1^+)' e^{-j\beta l_1}$$

$$V_1^- = (V_1^-)' e^{+j\beta l_1}$$

$$S_{11} = \frac{V_1^-}{V_1^+} = \frac{(V_1^-)' e^{+j\beta l_1}}{(V_1^+)' e^{-j\beta l_1}} = S'_{11} e^{+j2\beta l_1}$$

$$\Rightarrow S'_{11} = S_{11} e^{-j2\beta l_1} = S_{11} e^{-j2\theta_1}$$

$$\therefore S'_{11} = S_{11} e^{-j2\theta_1}$$

**(b)  $S_{21}$  :**

$$V_2 = V_2^+ e^{+j\beta l_2} + V_2^- e^{-j\beta l_2} = (V_2^+)' + (V_2^-)'$$

$$\text{Here, } V_2^+ = 0$$

$$\text{Hence, } V_2 = (V_2^-)' = V_2^- e^{-j\beta l_2}$$

$$\Rightarrow V_2^- = (V_2^-)' e^{+j\beta l_2}$$

 From previous discussion in  $S_{11}$ ,

$$V_1^+ = (V_1^+)' e^{-j\beta l_1}$$


$$\therefore S_{21} = \frac{V_2^-}{V_1^+} = \frac{(V_2^-)' e^{+j\beta l_2}}{(V_1^+)' e^{-j\beta l_1}} = S'_{21} e^{+j(\beta l_2 + \beta l_1)}$$

$$\Rightarrow S'_{21} = S_{21} e^{-j(\beta l_2 + \beta l_1)}$$

$$\Rightarrow S'_{21} = S_{21} e^{-j(\theta_1 + \theta_2)} \quad (\text{looking at options (a) is correct})$$

**End of Solution**

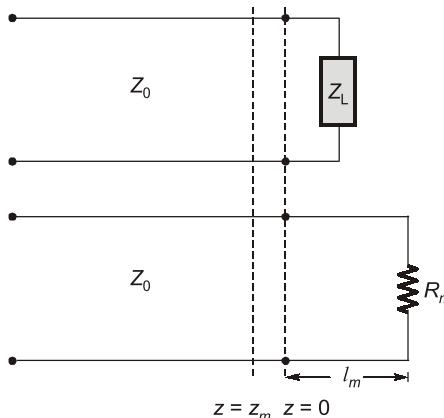- Q.52** The standing wave ratio on a  $50 \Omega$  lossless transmission line terminated in an unknown load impedance is found to be 2.0. The distance between successive voltage minima is 30 cm and the first minimum is located at 10 cm from the load.  $Z_L$  can be replaced by an equivalent length  $l_m$  and terminating resistance  $R_m$  of the same line. The value of  $R_m$  and  $l_m$ , respectively, are



- (a)  $R_m = 100 \Omega$ ,  $l_m = 20 \text{ cm}$       (b)  $R_m = 25 \Omega$ ,  $l_m = 20 \text{ cm}$   
 (c)  $R_m = 100 \Omega$ ,  $l_m = 5 \text{ cm}$       (d)  $R_m = 25 \Omega$ ,  $l_m = 5 \text{ cm}$

[2 Marks : MSQ]

**Ans.** (b, c)

Given  $S = 2$ ,  $Z_{\min} = 10 \text{ cm}$ ,  $Z_0 = 50 \Omega$

$$\text{As we know that, } |\Gamma| = \frac{S-1}{S+1} = \frac{2-1}{2+1} = \frac{1}{3}$$

Now, distance between successive voltage minima = 30 cm

$$\Rightarrow \frac{\lambda}{2} = 30 \text{ cm}$$

$$\Rightarrow \lambda = 60 \text{ cm}$$

Also, for minima,

$$2\beta Z_{\min} = (2n + 1)\pi + \theta_\Gamma$$

At  $n = 0$ , 1st minima,  $Z_{\min} = 10 \text{ cm}$

$$\frac{4\pi}{\lambda} Z_{\min} = \pi + \theta_\Gamma$$

$$\Rightarrow \frac{4\pi}{60} * 10 = \pi + \theta_\Gamma$$

$$\Rightarrow \frac{2\pi}{3} - \pi = \theta_\Gamma$$

$$\Rightarrow \theta_\Gamma = \frac{-\pi}{3} \quad \therefore \Gamma = \frac{1}{3} \angle -60^\circ$$

$$\text{Now, } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$\Rightarrow$ 

$$Z_L = Z_0 \left[ \frac{1 + \Gamma}{1 - \Gamma} \right]$$

 $\Rightarrow$ 

$$Z_L = 50 \left[ \frac{1 + 0.33e^{-j\frac{\pi}{3}}}{1 - 0.33e^{-j\frac{\pi}{3}}} \right]$$

 $\Rightarrow$ 

$$Z_L = 67.97 \angle -32.67^\circ$$

Now,

$$Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right]$$

 $\Rightarrow$ 

$$Z_{in} = 50 \left[ \frac{R_m + j50 \tan \beta l_m}{50 + jR_m \tan \beta l_m} \right]$$

Here,



$$Z_{in} = Z_L = 67.97 \angle -32.67^\circ$$

Going through options,

$R_m = 100 \Omega$  and  $L_m = 5 \text{ cm}$   
 and  $R_m = 25 \Omega$  and  $L_m = 20 \text{ cm}$

satisfy this identity, hence option (b) and (c) are

correct.

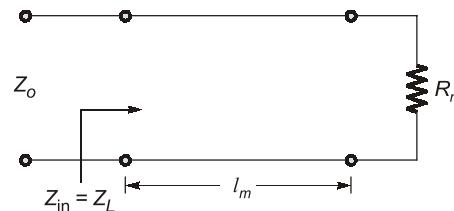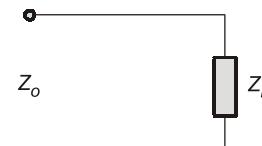
**End of Solution**
**Q.53** The electric field of a plane electromagnetic wave is

$$E = a_x C_{1x} \cos(\omega t - \beta z) + a_y C_{1y} \cos(\omega t - \beta z + \theta) \text{ V/m}$$

Which of the following combination(s) will give rise to a left handed elliptically polarized (LHEP) wave?

- (a)  $C_{1x} = 1, C_{1y} = 1, \theta = \pi/4$   
 (c)  $C_{1x} = 1, C_{1y} = 2, \theta = 3\pi/2$

- (b)  $C_{1x} = 2, C_{1y} = 1, \theta = \pi/2$   
 (d)  $C_{1x} = 2, C_{1y} = 1, \theta = 3\pi/4$

**[2 Marks : MSQ]**
**Ans.** (a, b, d)

$$\text{Given, } \vec{E} = \hat{a}_x C_{1x} \cos(\omega t - \beta z) + \hat{a}_y C_{1y} \cos(\omega t - \beta z + \theta)$$

 $at z = 0$ 


$$\vec{E} = C_{1x} \cos \omega t \hat{a}_x + C_{1y} \cos(\omega t + \theta) \hat{a}_y$$

Going by options,

$$\text{Option (a)} \quad \vec{E} = \cos \omega t \hat{a}_x + \cos(\omega t + \pi/4) \hat{a}_y$$

$$at t = 0, \omega t = 0, \vec{E} = \hat{a}_x + \frac{1}{\sqrt{2}} \hat{a}_y$$

$$at t = T/4, \omega t = \pi/2, \vec{E} = 0 - \frac{1}{\sqrt{2}} \hat{a}_y$$

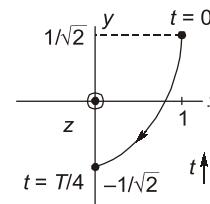 $\Rightarrow$  Hence, it is LHEP.


**Option (b)**

$$\vec{E} = 2\cos\omega t \hat{a}_x + \cos(\omega t + \pi/2) \hat{a}_y$$

at  $t = 0, \omega t = 0, \vec{E} = 2\hat{a}_x$

at  $t = T/4, \omega t = \pi/2, \vec{E} = -1\hat{a}_y$

$\Rightarrow$  Hence, it is LHEP.

**Option (c)**

$$\vec{E} = \cos\omega t \hat{a}_x + 2\cos(\omega t + 3\pi/2) \hat{a}_y$$

at  $t = 0, \omega t = 0, \vec{E} = \hat{a}_x$

at  $t = T/4, \omega t = \pi/2, \vec{E} = 2\hat{a}_y$

$\Rightarrow$  Hence, it is RHEP.

**Option (d)**




$$\vec{E} = 2\cos\omega t \hat{a}_x + \cos(\omega t + 3\pi/4) \hat{a}_y$$

at  $t = 0, \omega t = 0, \vec{E} = 2\hat{a}_x - \frac{1}{\sqrt{2}}\hat{a}_y$


at  $t = T/4, \omega t = \pi/2, \vec{E} = 0 - \frac{1}{\sqrt{2}}\hat{a}_y = \frac{-1}{\sqrt{2}}\hat{a}_y$


$\Rightarrow$  Hence, it is LHEP.

$\therefore$  Option (a), (b) and (d) are correct.

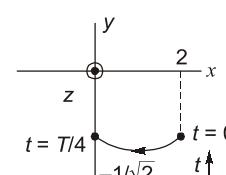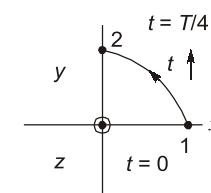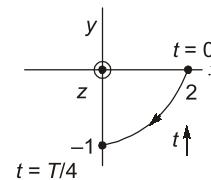
**End of Solution**

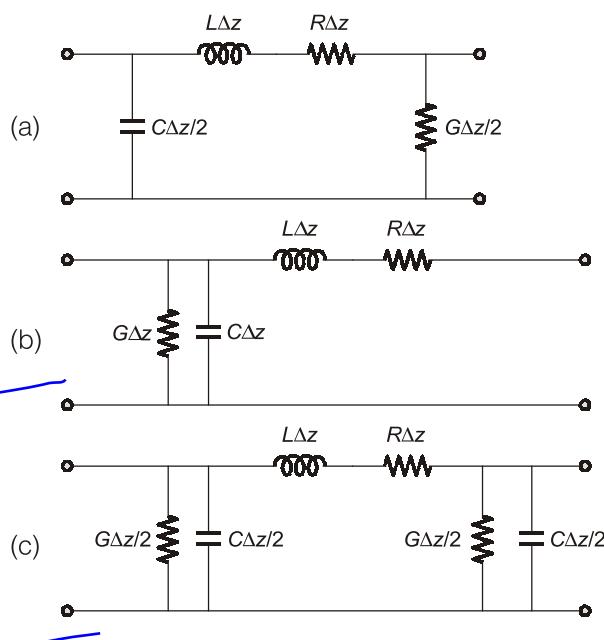- Q.54** The following circuit(s) representing a lumped element equivalent of an infinitesimal section of a transmission line is/are



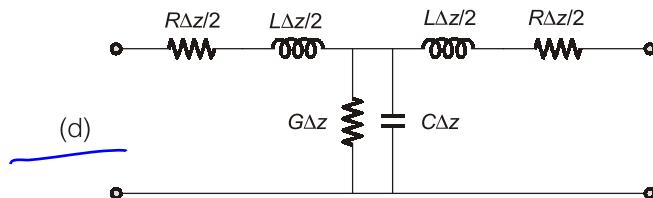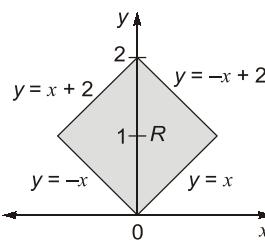

**[2 Marks : MSQ]**

Ans. (b, c, d)

**End of Solution**


**Q.55** The value of the integral  $\iint_R xy \, dx \, dy$  over the region  $R$ , given in the figure, is \_\_\_\_\_.

(rounded off to the nearest integer).


**[2 Marks : NAT]**

Ans. (0)

$$I = \iint_R xy \, dx \, dy$$

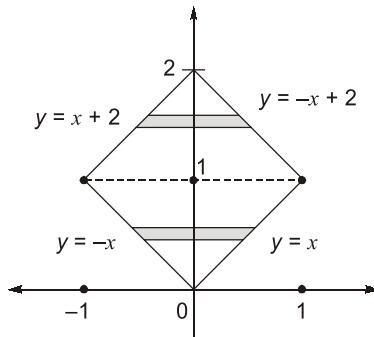

$$\begin{aligned}
 &= \int_{y=0}^1 \int_{x=-y}^y xy \, dx \, dy + \int_{y=1}^2 \int_{x=y-2}^{2-y} xy \, dx \, dy \\
 &= \int_0^1 y \left( \frac{x^2}{2} \right) \Big|_{-y}^y \, dy + \int_1^2 y \left( \frac{x^2}{2} \right) \Big|_{y-2}^{2-y} \, dy \\
 &= 0 + 0 = 0
 \end{aligned}$$

**End of Solution**

- Q.56** In an extrinsic semiconductor, the hole concentration is given to be  $1.5n_i$ , where  $n_i$  is the intrinsic carrier concentration of  $1 \times 10^{10} \text{ cm}^{-3}$ . The ratio of electron to hole mobility for equal hole and electron drift current is given as \_\_\_\_\_.  
(rounded off to two decimal places).

[2 Marks : NAT]

**Ans.** (2.25)

Given, intrinsic carrier concentration  $n_i = 1 \times 10^{10} \text{ cm}^{-3}$

Hole concentration,  $p = 1.5 \times n_i$

$$p = 1.5 \times 10^{10} \text{ cm}^{-3}$$

Given, electron and hole current are equal

$$I_p \text{ drift} = I_n \text{ drift}$$

$$pq \mu_p EA = nq \mu_n EA$$

$$1.5 \times 10^{10} \mu_p = n \mu_n$$

... (i)

But according to mass action law,

$$np = n_i^2$$

$$\therefore n = \frac{n_i}{1.5} = \frac{10^{10}}{1.5} \text{ cm}^{-3}$$

Put in equation (i)


$$\therefore 1.5 \times 10^{10} \mu_p = \frac{10^{10}}{1.5} \times \mu_n$$

$$\frac{\mu_n}{\mu_p} = 2.25$$

**End of Solution**

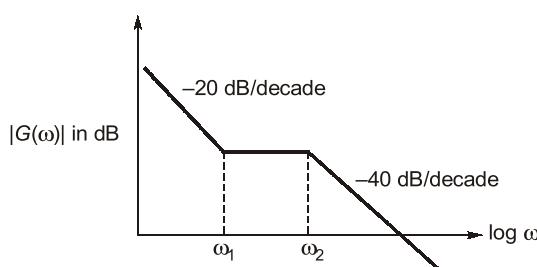- Q.57** The asymptotic magnitude Bode plot of a minimum phase system is shown in the figure.

The transfer function of the system is  $(s) = \frac{k(s+z)^a}{s^b(s+p)^c}$ , where  $k, z, p, a, b$  and  $c$  are positive constants. The value of  $(a + b + c)$  is \_\_\_\_\_.  
(rounded off to the nearest integer).



[2 Marks : NAT]

**Ans.** (4)

From the Bode magnitude plot, it is clear that there is one pole at origin,

$$\therefore b = 1$$

and at frequency  $\omega_1$ , system has a zero

$$\therefore a = 1$$

and at frequency  $\omega_2$ , system have two poles

$$\therefore c = 2$$


$$\therefore a + b + c = 1 + 1 + 2$$

$$a + b + c = 4$$

End of Solution

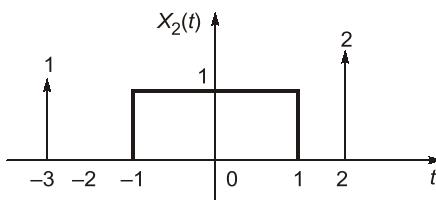**Q.58** Let  $x_1(t) = u(t + 1.5) - u(t - 1.5)$  and  $x_2(t)$  is shown in the figure below. For  $y(t) = x_1(t) * x_2(t)$ ,


the  $\int_{-\infty}^{\infty} y(t) dt$  is \_\_\_\_\_. (rounded off to the nearest integer).



[2 Marks : NAT]

**Ans. (15)**

$$x_1(t) = u(t + 1.5) - u(t - 1.5)$$

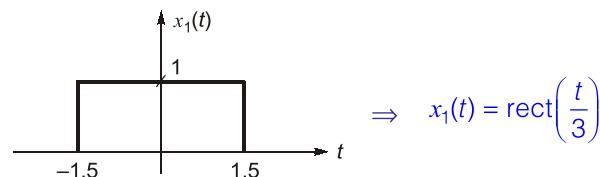

$$x_1(t) = \text{rect}\left(\frac{t}{3}\right) \xrightarrow{\text{FT}} 3\text{Sa}(1.5\omega)$$

$$\text{Now, } x_2(t) = \delta(t + 3) + \text{rect}\left(\frac{t}{2}\right) + 2\delta(t - 2)$$

Taking Fourier transform

$$X_2(\omega) = e^{3j\omega} + 2\text{Sa}(\omega) + 2e^{-2j\omega}$$

$\therefore$

$$y(t) = x_1(t) * x_2(t)$$

$$Y(\omega) = X_1(\omega) \cdot X_2(\omega)$$

We know,

$$Y(\omega) = \int_{-\infty}^{\infty} y(t) \cdot e^{-j\omega t} \cdot dt$$

$\therefore$

$$\int_{-\infty}^{\infty} y(t) = Y(0)$$

$\therefore$


$$Y(0) = X_1(0) \cdot X_2(0) \\ = 3[1 + 2 + 2] = 15$$

End of Solution

- Q.59** Let  $X(t)$  be a white Gaussian noise with power spectral density  $\frac{1}{2}$  W/Hz. If  $X(t)$  is input to an LTI system with impulse response  $e^{-t}u(t)$ . The average power of the system output is \_\_\_\_\_ W. (Rounded off to two decimal place).

[2 Marks : NAT]

**Ans.** (0.25)

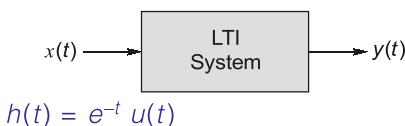

**Given:** Input PSD

$$\Rightarrow S_X(f) = \frac{1}{2} \text{ W/Hz}$$

We know output PSD,

$$S_Y(f) = S_X(f)|H(f)|^2$$

$$S_Y(f) = \frac{1}{2}|H(f)|^2$$

$$\begin{aligned} \text{Power } [y(t)] &= \int_{-\infty}^{\infty} S_Y(f) df = \int_{-\infty}^{\infty} \frac{1}{2}|H(f)|^2 df \\ &= \frac{1}{2} \int_{-\infty}^{\infty} H^2(f) df = \frac{1}{2} \int_0^{\infty} e^{-2f} dt \\ &= \frac{1}{2} \times \frac{1}{2} = \frac{1}{4} = 0.25 \text{ W} \end{aligned}$$

**End of Solution**


- Q.60** A transparent dielectric coating is applied to glass ( $\epsilon_r = 4$ ,  $\mu_r = 1$ ) to eliminate the reflection of red light ( $\lambda_0 = 0.75 \mu\text{m}$ ). The minimum thickness of the dielectric coating, in  $\mu\text{m}$ , that can be used is \_\_\_\_\_ (rounded off to two decimal places).

[2 Marks : NAT]

**Ans.** (0.133)

For no reflection, impedance must be matched.

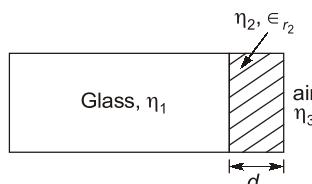Hence,  $\eta_2$  acts like a quarter wave impedance transformer.



So,

$$(i) \quad \eta_2 = \sqrt{\eta_1 \cdot \eta_3} \Rightarrow \epsilon_{r2} = \sqrt{\epsilon_{r1} \cdot \epsilon_{r3}} \Rightarrow \epsilon_{r2} = 2$$

(ii) For impedance matching,

$$d = (2n+1)\frac{\lambda}{4}; \quad n = 0, 1, 2, \dots$$

$$\lambda = \frac{\lambda_0}{\sqrt{\epsilon_r}} = \frac{\lambda_0}{\sqrt{\epsilon_{r_2}}}$$

$$\text{Here, } \lambda = \frac{0.75 \times 10^{-6}}{\sqrt{2}} = 0.53 \times 10^{-6}$$

Hence, for minimum distance,  $n = 0$

$$\text{So, } d = \frac{\lambda}{4} = \frac{0.53 \times 10^{-6}}{4} = 0.133 \mu\text{m}$$

**End of Solution**

- Q.61** In a semiconductor device, the Fermi-energy level is 0.35 eV above the valence band energy. The effective density of states in the valence band at  $T = 300 \text{ K}$  is  $1 \times 10^{19} \text{ cm}^{-3}$ . The thermal equilibrium hole concentration in silicon at  $400 \text{ K}$  is \_\_\_\_\_  $\times 10^{13} \text{ cm}^{-3}$ . (rounded off to two decimal places).
- Given  $kT$  at  $300 \text{ K}$  is 0.026 eV.

**[2 Marks : NAT]**

**Ans. (63.36)**

Given,  $E_F - E_V = 0.35 \text{ eV}$  [Considering it is given at  $400 \text{ K}$ ]

Also,  $V_{T_1} = kT_1 = 0.026 \text{ eV}$  at  $T_1 = 300 \text{ K}$

$$\therefore \frac{V_{T_1}}{V_{T_2}} = \frac{T_1}{T_2} \Rightarrow V_{T_2} = \frac{T_2}{T_1} \times V_{T_1}$$

$$\therefore V_{T_2} = \frac{400}{300} \times 0.026$$

$$V_{T_2} = 0.03466 \text{ eV}$$
 at  $T_2 = 400 \text{ K}$

Now,  $N_v = 1 \times 10^{19}/\text{cm}^3$  at  $T_1 = 300 \text{ K}$

$$N_v \propto T^{3/2}$$

$$\frac{N_{V_2}}{N_{V_1}} = \left( \frac{T_2}{T_1} \right)^{3/2}$$

$$N_{V_2} = \left( \frac{T_2}{T_1} \right)^{3/2} N_{V_1} \quad (\because T_2 = 400 \text{ K})$$

$$= \left( \frac{400}{300} \right)^{3/2} N_{V_1}$$

$$N_{V_2} = 1.5396 \times 10^{19}/\text{cm}^3$$

Now, hole concentration at  $400 \text{ K}$  is given as

$$p = N_v e^{-(E_F - E_V)/kT_2} = 1.5396 \times 10^{19} \times e^{-0.35 \text{ eV}/0.03466 \text{ eV}}$$

$$p = 63.36 \times 10^{13} \text{ cm}^{-3}$$

**End of Solution**


- Q.62** A sample and hold circuit is implemented using a resistive switch and a capacitor with a time constant of  $1 \mu\text{s}$ . The time for sampling switch to stay closed to charge a capacitor adequately to a full scale voltage of  $1 \text{ V}$  with 12-bit accuracy is \_\_\_\_\_  $\mu\text{s}$ .  
(rounded off to two decimal places)

[2 Marks : NAT]

**Ans.** (8.3177)

**Given:** Time constant ( $\tau$ ) of  $1 \mu\text{s}$ .

Full scale voltage =  $1 \text{ V}$

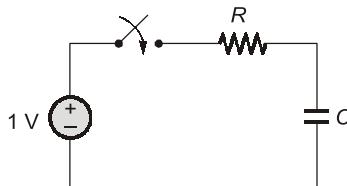

The voltage across capacitor is given as

$$V_c(t) = V_{in}(1 - e^{-t/\tau})$$

$$\therefore V_c(t) = (1 - e^{-t/1 \mu\text{s}}) \quad \dots(i)$$

To calculate the voltage to stay closed to charge capacitor adequately to a full scale voltage with 12-bit accuracy is given by

$$V_c(t) = V_{ref} \left[ 1 - \frac{1}{2^n} \right]$$

$n$  = Number of bit = 12


$$\therefore V_c(t) = \left[ 1 - \frac{1}{4096} \right] \quad \dots(ii)$$

Comparing equations (i) and (ii), we get,

$$\begin{aligned} e^{-t/1 \mu\text{s}} &= \frac{1}{4096} \\ -\frac{t}{1 \mu\text{s}} &= \ln \left\{ \frac{1}{4096} \right\} \\ t &= 8.3177 \mu\text{s} \end{aligned}$$

**End of Solution**

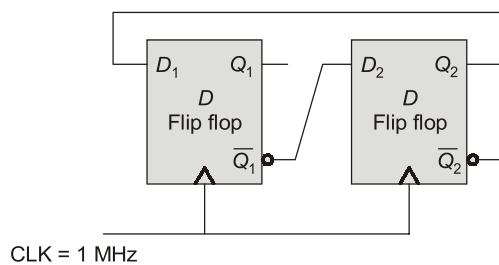- Q.63** In a given sequential circuit, initial states are  $Q_1 = 1$  and  $Q_2 = 0$ . For a clock frequency of  $1 \text{ MHz}$ , the frequency of signal  $Q_2$  in  $\text{kHz}$ , is \_\_\_\_\_.  
(rounded off to the nearest integer).



[2 Marks : NAT]

Ans. (250)


| Clk     | $D_1 = Q_2$ | $D_2 = \bar{Q}_1$ | $Q_1$ | $Q_2$ |
|---------|-------------|-------------------|-------|-------|
| Initial |             |                   | 1     | 0     |
| 1       | 0           | 0                 | 0     | 0     |
| 2       | 0           | 1                 | 0     | 1     |
| 3       | 1           | 1                 | 1     | 1     |
| 4       | 1           | 0                 | 1     | 0     |

Therefore, the given counter is having MOD-4

$$\therefore \text{The frequency of signal } Q_2 = \frac{f_i}{4} = \frac{1000}{4} \text{ kHz} = 250 \text{ kHz}$$


End of Solution

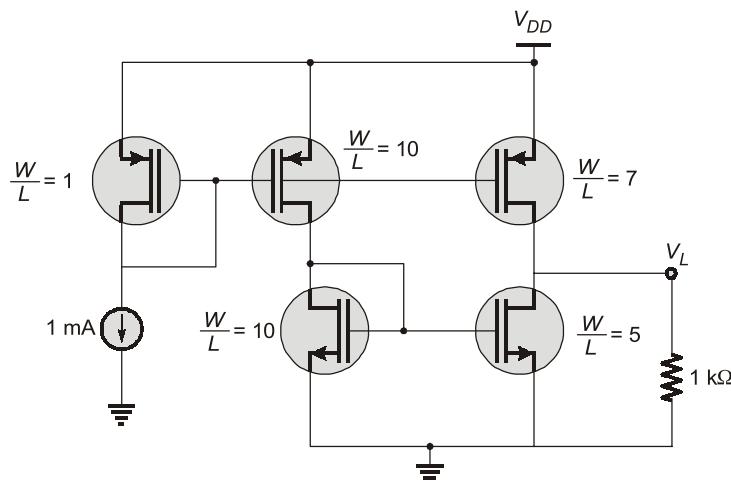- Q.64** In the circuit below, the voltage  $V_L$  is \_\_\_\_\_ V.  
 (rounded off to two decimal places)



[2 Marks : NAT]

Ans. (2)

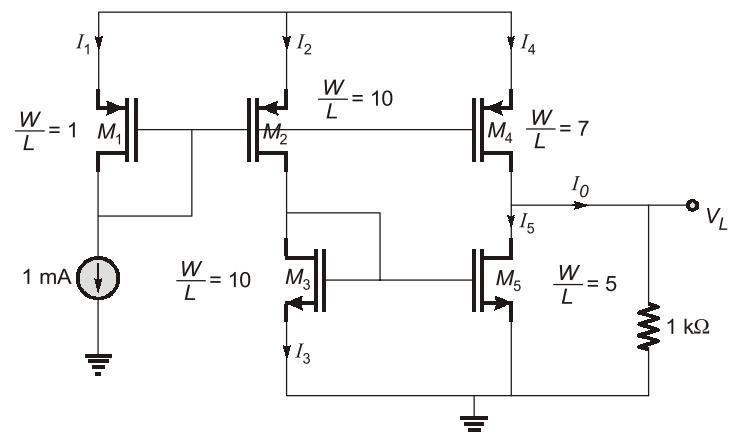

We know,

$$I_D \propto \left(\frac{W}{L}\right)$$

$$I_1 = 1 \text{ mA}$$

$$I_2 = \frac{10}{1} \times 1 = 10 \text{ mA}$$

$$I_3 = 10 \text{ mA}$$

$$I_4 = 7 \text{ mA}$$

$$I_5 = 5 \text{ mA}$$

$$I_0 = I_4 - I_5 = 7 - 5 = 2 \text{ mA}$$

$$V_L = 2 \times 1 = 2V$$

**End of Solution**

- Q.65** The frequency of occurrence of 8 symbols (*a-h*) is shown in the table below. A symbol is chosen and it is determined by asking a series of “yes/no” questions which are assumed to be truthfully answered. The average number of questions when asked in the most efficient sequence, to determine the chosen symbol, is \_\_\_\_\_. (rounded off to two decimal places).

| Symbols                 | <i>a</i>      | <i>b</i>      | <i>c</i>      | <i>d</i>       | <i>e</i>       | <i>f</i>       | <i>g</i>        | <i>h</i>        |
|-------------------------|---------------|---------------|---------------|----------------|----------------|----------------|-----------------|-----------------|
| Frequency of occurrence | $\frac{1}{2}$ | $\frac{1}{4}$ | $\frac{1}{8}$ | $\frac{1}{16}$ | $\frac{1}{32}$ | $\frac{1}{64}$ | $\frac{1}{128}$ | $\frac{1}{128}$ |

**[2 Marks : NAT]**
**Ans. (1.984)**

The average number of questions when asked in the most efficient sequence, to determine the chosen symbol = min possible number of questions per symbol (*H*)

$$\begin{aligned}
 H &= \sum_i P_x(x_i) \log_2 \frac{1}{P_x(x_i)} \\
 &= \frac{1}{2} \log_2 2 + \frac{1}{4} \log_2 4 + \frac{1}{8} \log_2 8 + \frac{1}{16} \log_2 16 + \frac{1}{32} \log_2 32 + \frac{1}{64} \log_2 64 + 2 \times \frac{1}{128} \log_2 128 \\
 &= 1.984 \frac{\text{Questions}}{\text{Symbol}}
 \end{aligned}$$

**End of Solution**
